

→ Subject Name :- BEEE (Basic Electrical and Electronics Engineering)

→ Subject code :- BT-104

→ Faculty :- Iqbal Khan

→ Book :- V.N Mittal, J.B Gupta

→ Units :-

Unit 1 :- DC Circuit

Unit 2 :- AC Circuit

Unit 3 :- Transformer and Magnetic Circuit

Unit 4 :- Electrical Machine

Unit 5 :- Basic Electronics

Unit 1 (DC Circuit)

Topics :-

- 1) Ohm's Law
- 2) series and parallel combination of Resistance
- 3) KCL and KVL
- 4) Mesh Analysis method
- 5) Nodal Analysis method
- 6) source conversion Technique
- 7) Dependent and Independent source
- 8) Ideal voltage/current source and practical voltage source
- 9) Thevenin's Theorem

- 10.) Superposition theorem
 11.) Star Delta conversion.

Date
 22/03/25

1-1

APL-T8

*.) Electric Current :-

The current flowing through a conductor is said to be one ampere if one coulomb of charge flows in one second.

$$I = Q/t$$

where,
 $Q = \text{charge}$
 $t = \text{time}$

*.) Potential or Voltage :-

The amount of work done in carrying unit positive charge from A to B along any path b/w two points is called Electric potential.

$$1 \text{ Vol} = \frac{1 \text{ Joule}}{1 \text{ Coulomb}}$$

*.) Resistance :-

Resistance is the property of material by virtue of which it opposes the flow of electrons through the material. It restricts the flow of electric current through the material.

The unit of Resistance is ohm (Ω).

$$R = \frac{V}{I}$$


where,

V = Voltage

I = Current

* Resistance in series :-

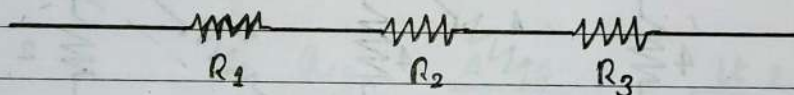When the resistances are connected to end to end, so that they form only one path of the flow of current.




$$R_{eq} (R) = R_1 + R_2 + R_3$$

* Resistance in parallel :-

When a number of ~~res~~ resistances are connected in such a way that one end of each of them is joined to a common point and the other ends being joined to another common point.

Let the R_1, R_2

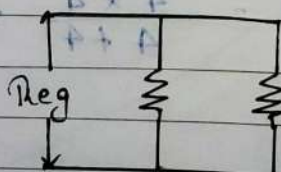


$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_{eq}} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Qn.) find total Resistance across A & B.





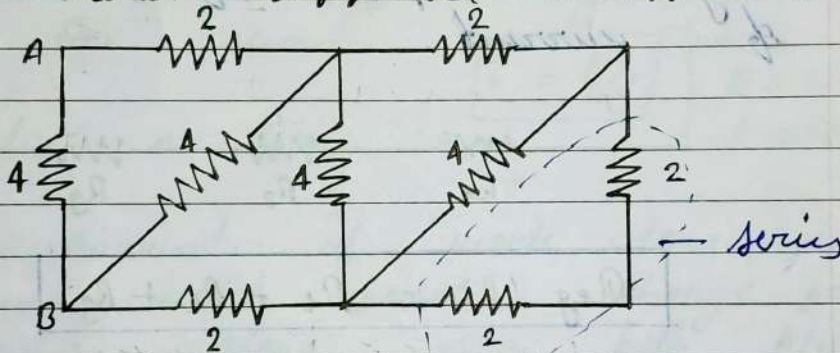


$$R_{eq} = 2 + 2 = 4$$

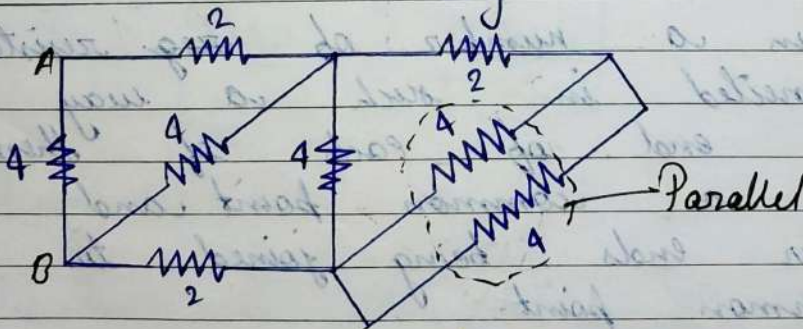

$$R_{eq} = \frac{1}{\frac{1}{4} + \frac{1}{4}} = 2$$
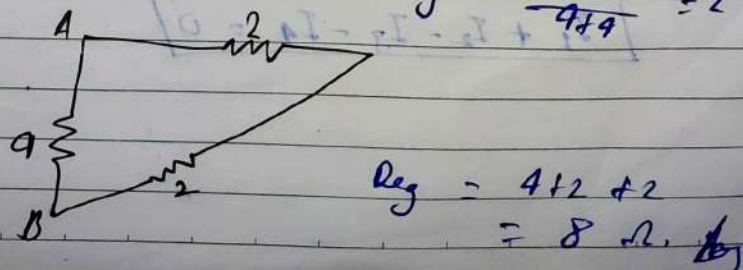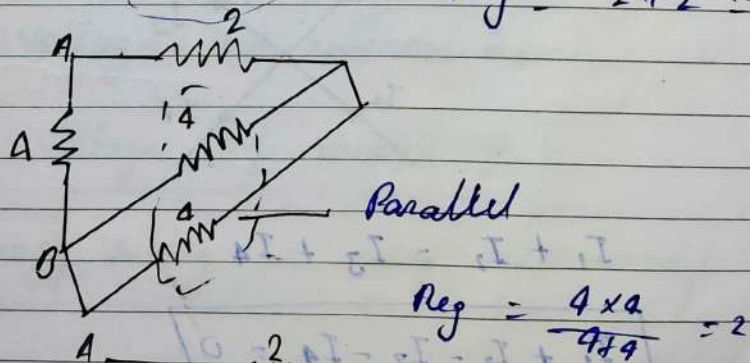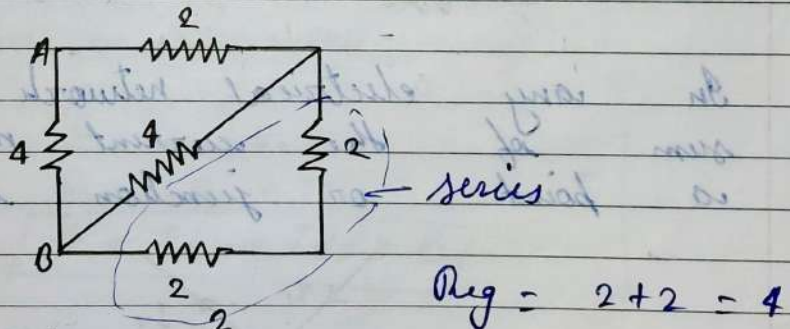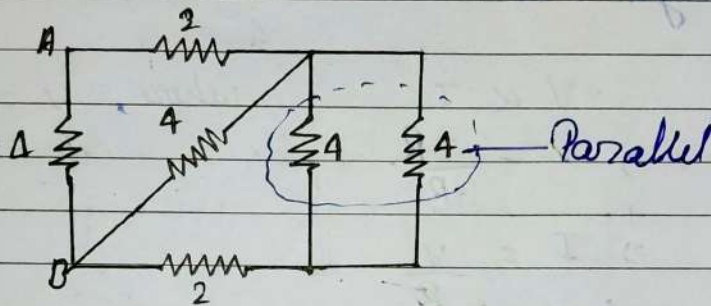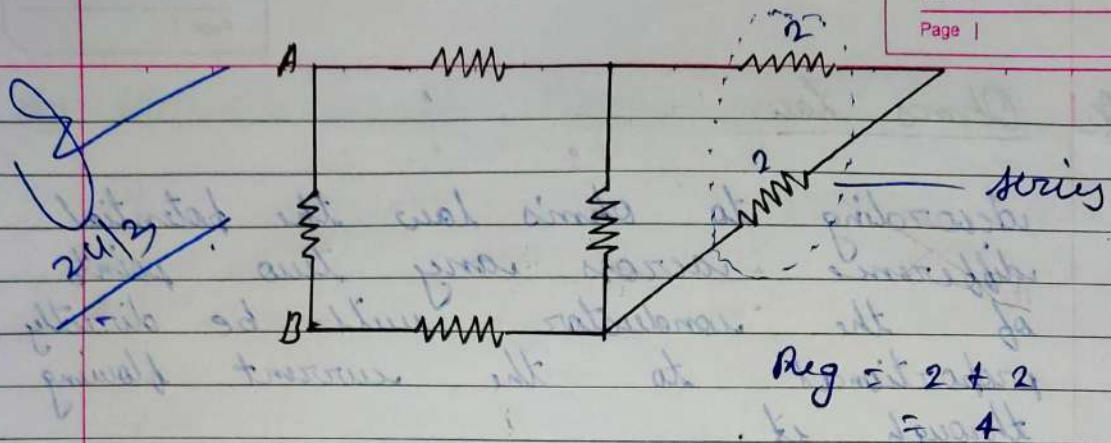
$$R_{eq} = \frac{4 \times 4}{4 + 4} = \frac{16}{8} = 2$$



*.) Ohm's Law :-

According to Ohm's law the potential difference across any two points of the conductor will be directly proportional to the current flowing through it.

$$V \propto I$$


$$\Rightarrow V = IR$$

$$\Rightarrow I = \frac{V}{R}$$

where, V = voltage - ^{unit} volt
 I = current - Amp

*.) KCL (Kirchhoff's Current law) :-

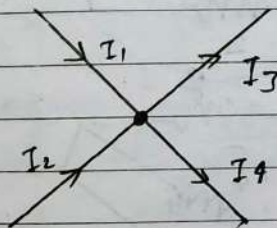In any electrical network the algebraic sum of the current meeting at a point or junction is zero.




$$I_1 + I_2 = I_3 + I_4$$

$$\boxed{I_1 + I_2 - I_3 - I_4 = 0}$$

★) KVL (Kirchhoff's Voltage Law) :-

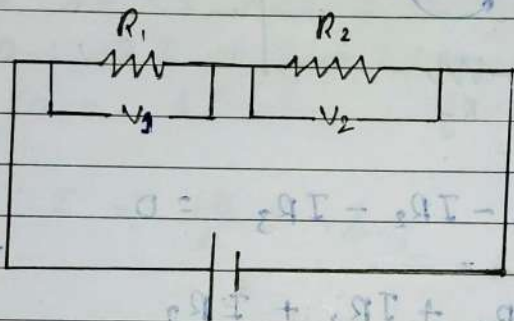The algebraic sum of the products of current and resistance in each of the conductor, in any closed path (or mesh) in a network plus the algebraic sum of the EMF (electromotive force) in that path is zero.



According to KVL law,

$$E = V_1 + V_2$$

$$E = IR_1 + IR_2$$

$$E - IR_1 - IR_2 = 0$$



V_1 = Voltage Drop across R_1

V_2 = Voltage Drop across R_2

$$\boxed{\text{Energy supply} = \text{Energy consumed}}$$

★ Mesh Analysis Method OR Loop Analysis method OR KVL Method :-

Mesh Analysis method based on KVL method

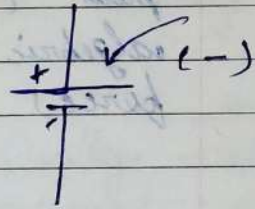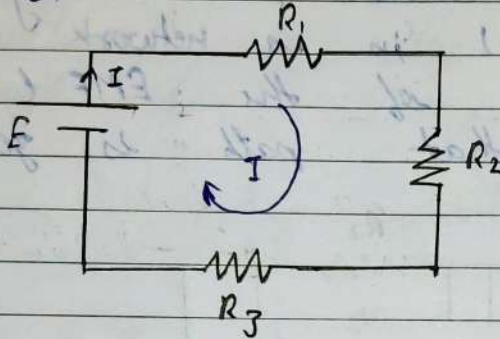


$$E - IR_1 - IR_2 - IR_3 = 0$$

$$\Rightarrow E = IR_1 + IR_2 + IR_3$$

$$\Rightarrow E = I(R_1 + R_2 + R_3)$$
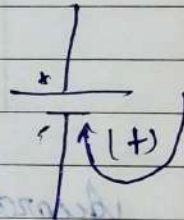
$$\Rightarrow I = \frac{E}{R_1 + R_2 + R_3}$$



find power across R_1 , R_2 , R_3


$$P = I^2 R$$

$$P = I^2 R_1$$

$$P = I^2 R_2$$

$$P = I^2 R_3$$

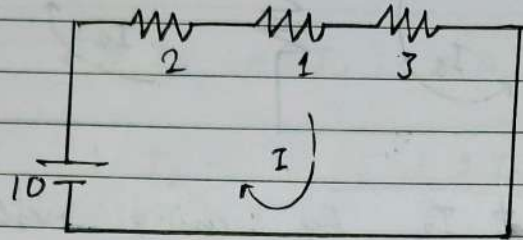Ques) find current in this circuit by using Mesh method ;



Solu)


$$10 - 2I - I - 3I = 0$$

$$\Rightarrow 10 = 2I + I + 3I$$

$$\Rightarrow 10 = 6I$$

$$\therefore I = \frac{10}{6} \text{ A} \quad \underline{\underline{\text{Ans}}}$$

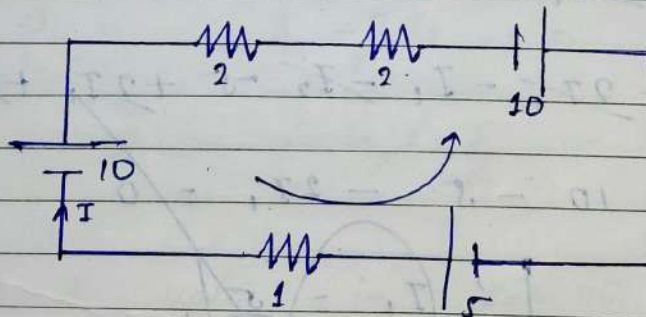Ques) find current in this circuit by using Mesh Analysis Method :-




Solu)

$$-5 - 10 - 10 - 2I - 2I - I = 0$$

$$\Rightarrow -25 - 5I = 0$$

$$\therefore I = -5 \quad \underline{\underline{\text{Ans}}}$$

Qn.)

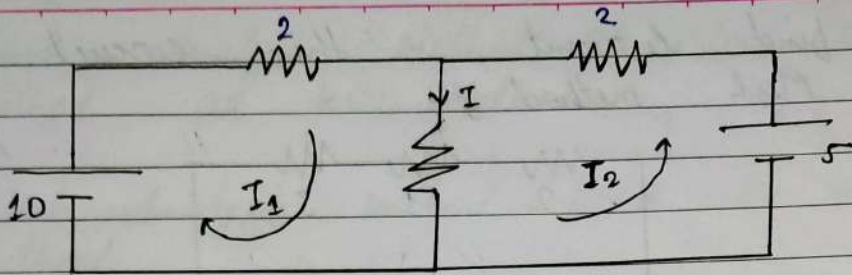

- ① find I_1 & I_2 by using mesh analysis method?
 (i) find current across 1Ω resistance?
 (ii) find power across 1Ω resistance?

Soln.

$$10 - 2I_1 - 1(I_1 + I_2) = 0 \quad \text{--- (1)}$$

$$5 - 2I_2 - 1(I_2 + I_1) = 0 \quad \text{--- (2)}$$

subtracting

Adding eqⁿ (1) and (2)

$$10 - 2I_1 - I_1 - I_2 + 5 - 2I_2 - I_2 + I_1 = 0$$

$$10 - 2I_1 - I_1 - I_2 - 5 + 2I_2 + I_2 - I_1 = 0$$

$$10 - 5 - 2I_1 = 0$$

$$\therefore I_1 = \frac{5}{2}$$

Putting the value in eqⁿ (1), we get,

$$5 - 2 \times \frac{5}{2} - I_2 + \frac{5}{2} = 0$$

$$5 - 5 - I_2 + \frac{5}{2} = 0$$

$$I_2 = \frac{5}{2}$$

$$\begin{array}{rclcl} 10 & -2I_1 & -1(I_1 + I_2) & = & 0 \\ -5 & -2I_2 & -1(I_2 + I_1) & = & 0 \\ \hline & + & + & & \end{array}$$

$$5 + 2I_2 - 2I_1 = 0 \quad \text{--- (11)}$$

$$\therefore I_1 = \frac{5 + 2I_2}{2} \quad \text{--- (12)}$$

Put the value in eqn (1)

$$10 - \cancel{1} \left(\frac{5 + 2I_2}{2} \right) - \frac{5 + 2I_2}{2} - I_2 = 0$$

$$\Rightarrow 10 - 5 - 2I_2 - \frac{5}{2} - \frac{I_2}{2} + \frac{I_2}{2} = 0$$

$$\Rightarrow 5 - 4I_2 - \frac{5}{2} = 0$$

$$\Rightarrow \frac{10 - 8I_2 - 5}{2} = 0$$


$$\Rightarrow \frac{5 - 8I_2}{2} = 0$$

$$\Rightarrow \therefore I_2 = \frac{5}{8} = 0.625$$

$$\begin{aligned} \textcircled{ii} \quad \therefore I &= I_1 + I_2 \\ &= 0.625 + 3.125 \\ &= 3.75 \end{aligned}$$

$$\begin{aligned} \textcircled{iii} \quad P &= I^2 R \\ &= (3.75)^2 \times 1 \\ &= 14.0625 \text{ Watt.} \end{aligned}$$

Ques

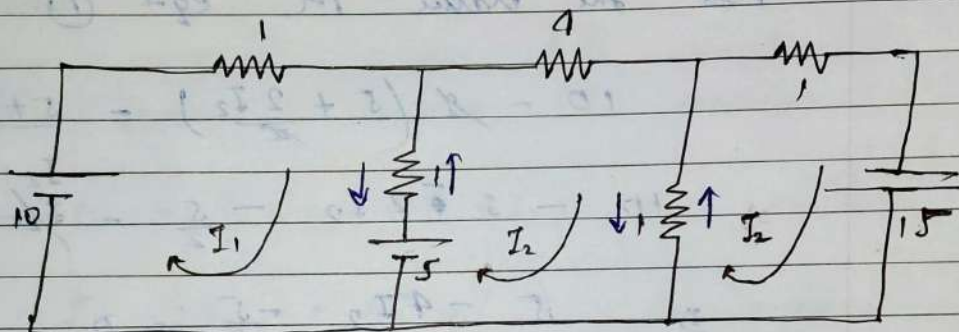

- ① find I_1, I_2 & I_3
- ② find current across 4Ω resistance.
- ③ Power across 4Ω resistance

Soln

~~$$10 - I_1 - 1(I_1 - I_2) - 5 = 0$$

$$10 - I_1 - 5 - 1(I_1 - I_2) = 0$$~~

$$10 - I_1 - 1(I_1 - I_2) - 5 = 0$$

$$5 - 1(I_1 - I_2) - 4I_2 - 1(I_2 - I_3) = 0$$

$$15 - I_3 - 1(I_3 - I_2) = 0$$

$$5 - 2I_1 + I_2 = 0 \quad \text{--- (i)}$$

$$5 - 6I_2 + I_3 + I_1 = 0 \quad \text{--- (ii)}$$

$$15 - 2I_3 + I_2 = 0 \quad \text{--- (iii)}$$

$$\begin{aligned}
 x &= 5.83 \quad 4 \\
 y &= 3.33 \quad 3 \\
 z &= 8.16 \quad 9
 \end{aligned}$$

(ii)

current across $4\Omega = 3 \text{ Amp}$

$$\begin{aligned}
 V_2 &= 12 \text{ V} \\
 &= 12 \times 1 \\
 &= 12 \text{ V}
 \end{aligned}$$

(iii)


$$P = I^2 R$$

$$= (3)^2 \times 4$$

$$= 13 \text{ Watt}$$

$$I = \frac{200}{9}$$

(Q.11)

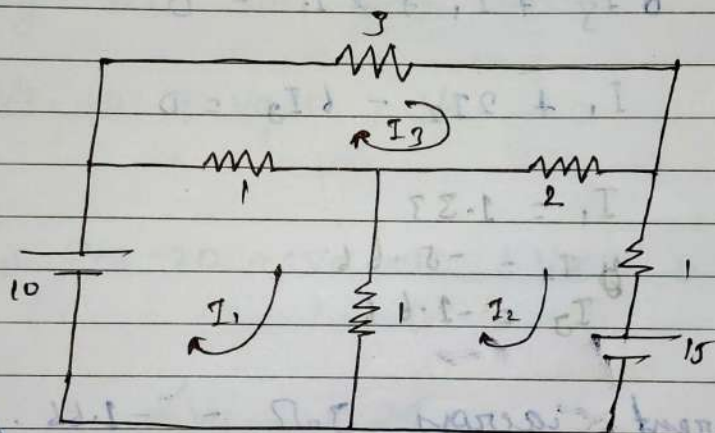find current across 3Ω resistance?

Soln,

$$10 - 1(I_1 - I_3) - (I_1 - I_2) = 0 \quad \text{--- (i)}$$

$$-15 - 1(I_2 - I_1) - 2(I_2 - I_3) - I_2 = 0$$

--- (ii)

$$3I_3 - 1(I_3 - I_1) - 2(I_3 - I_2) = 0 \quad \text{--- (iii)}$$

from eqn (i)

$$10 - I_1 + I_3 - I_2 + I_2 = 0$$

$$10 - 2I_1 + I_2 + I_3 = 0$$

$$-2I_1 + I_2 + I_3 = -10 \quad \text{--- (iv)}$$

from eqⁿ (i)

$$-15 - I_2 + I_1 - 2I_2 + 2I_3 - I_2 = 0$$

$$\Rightarrow -15 - 3I_2 + I_1 + 2I_3 = 0$$

$$\Rightarrow I_1 - 3I_2 + 2I_3 = 15$$

from eqⁿ (ii)

$$-3I_3 - I_3 + I_1 - 2I_3 + 2I_2 = 0$$

$$\Rightarrow -6I_3 + I_1 + 2I_2 = 0$$

$$\Rightarrow I_1 + 2I_2 - 6I_3 = 0$$

$$I_1 = 1.33$$

$$I_2 = -5.66$$

$$I_3 = -1.66$$

current across $3\Omega = -1.66 \text{ A}$


*.) Node Analysis Method :-

Node analysis provides a general procedure for analysing circuits using node voltages as the circuit variable.

It is based on Kirchhoff's current law (KCL)

Node is defined as the point where two or more than two elements are joined together.

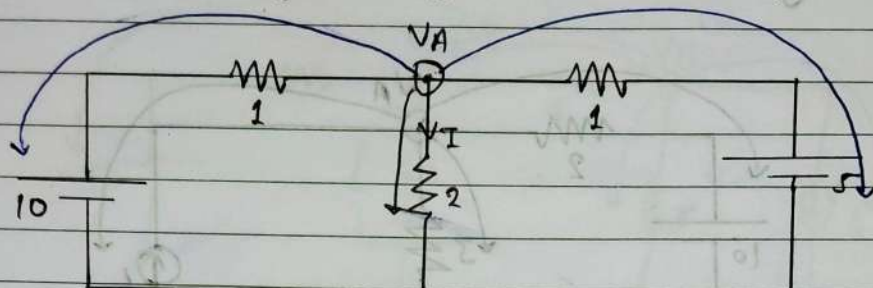Ques) find current and power across 2Ω resistance by using Nodal Analysis method?



Solu $\Rightarrow$ Apply KCL at Node No. 1

$$\frac{V_A - 10}{1} + \frac{V_A - 5}{1} + \frac{V_A}{2} = 0$$

$$\Rightarrow 2V_A - 20 + 2V_A - 10 + V_A = 0$$

$$\Rightarrow 5V_A = 30$$

$$\Rightarrow V_A = 6 \text{ V}$$

$\therefore$ Current across 2Ω resistance,

$$I_2 = \frac{V_A}{2} = \frac{6}{2} = 3 \text{ A}$$

$\therefore$ Power across 2Ω resistance,

$$P = I^2 R$$


$$= (3)^2 \times 2$$

$$= 18 \text{ watt}$$

Ans

Ques) Find current across 3Ω resistance by using Nodal analysis method?

Soln

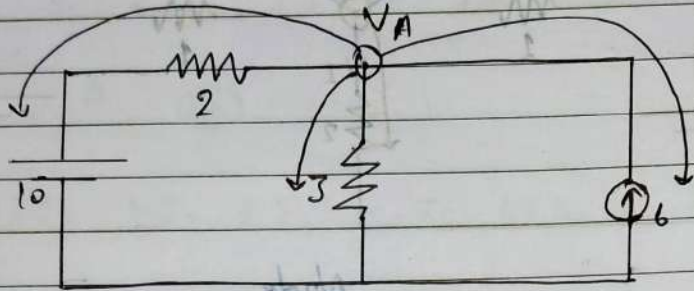

Soln Apply KCL on Node No. 1,

$$\frac{V_A - 10}{2} + \frac{V_A}{3} - 6 = 0$$

$$\Rightarrow \frac{3V_A - 30 + 2V_A - 36}{6} = 0$$

$$\Rightarrow \frac{5V_A - 66}{6} = 0$$

$$\Rightarrow 5V_A = 66$$


$$\therefore V_A = \frac{66}{5}$$

Now, current across 3Ω resistance,

$$I = \frac{V_A}{3} = \frac{\frac{66}{5}}{3} = \frac{22}{5} \text{ A}$$

Qn. 3.)

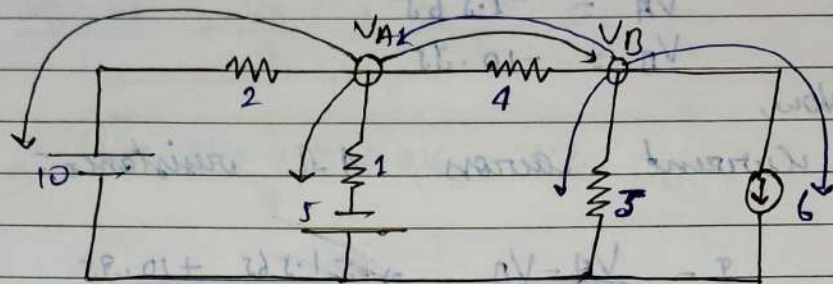find current across 4Ω resistance by using Node Analysis method?



Soln. Apply KCL on Node No. 1,

$$\frac{V_A - 10}{2} + \frac{V_A + 5}{1} + \frac{V_A - V_B}{4} = 0$$

$$\Rightarrow \frac{2V_A - 20 + 4V_A + 20 + V_A - V_B}{4} = 0$$

$$\Rightarrow \frac{7V_A - V_B}{4} = 0$$

$$\Rightarrow 7V_A - V_B = 0$$

Apply KCL on Node No. 2,

$$\frac{V_B - V_A}{4} + \frac{V_B}{3} + 6 = 0$$

$$\Rightarrow \frac{3V_B - 3V_A - 4V_B + 72}{12} = 0$$

$$\Rightarrow -3V_A + 7V_B = -72$$

Solving eqn ① & ②

$$V_A = -1.565$$

$$V_B = -10.95$$

Now,


current across 4Ω resistance,

$$I = \frac{V_A - V_B}{4} \Rightarrow \frac{-1.565 + 10.95}{4}$$

$$\Rightarrow I \Rightarrow 2.34$$



Qn-1

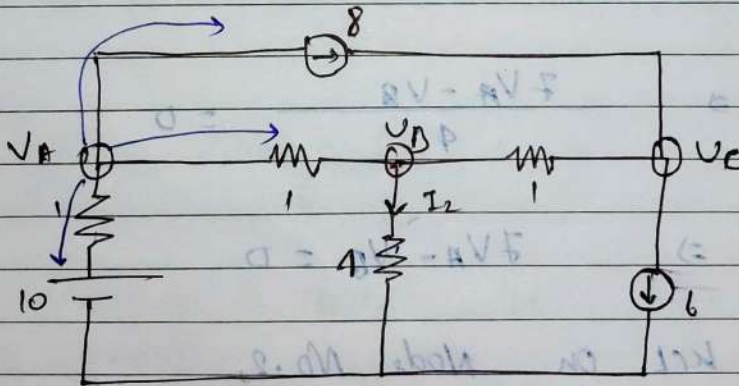

find current across 4Ω resistance by using Nodal Analysis method?

Soln

$$\frac{V_A - 10}{1} + \frac{V_A - V_B}{1} + \frac{8}{1} = 0$$

$$\frac{V_A - 10 + V_A - V_B + 8}{1} = 0$$

$$2V_A - V_B + 0V_C = 2$$

or,

$$\frac{V_B - V_A}{1} + \frac{V_B}{4} + \frac{V_B - V_C}{1} = 0$$

$$\Rightarrow \frac{4V_B - 4V_A + V_B + 4V_B - 4V_C}{4} = 0$$

$$\Rightarrow -4V_A + 9V_B - 4V_C = 0$$

or

$$\Rightarrow \frac{V_C - V_B}{1} + 6 - 8 = 0$$

$$\Rightarrow \frac{V_C - V_B + 6 - 8}{1} = 0$$

$$-8 + V_C - V_B + 6 - 8 + 4V_A - 4V_A + 0 - 4V_C = 0$$

$$\Rightarrow V_C - V_B = 5/2$$

$$-8 + 3 + 4V_A - V_B + V_C = 0$$

$$V_A = 3$$

$$V_B = 4$$

$$V_C = 6$$

Now,


current across 4Ω resistance,

$$I = \frac{V_B}{4}$$

$$I = \frac{4}{4} = 1 \text{ A}$$

Ans)

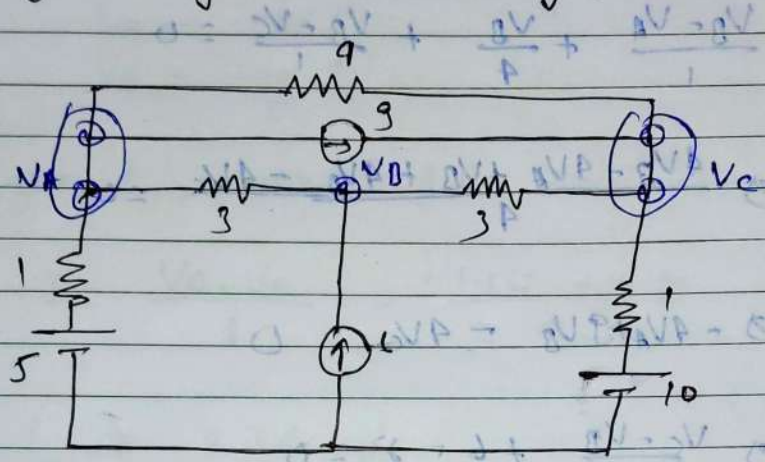find current across 4Ω resistance by using Nodal Analysis method



Solving

$$\frac{V_a - 5}{1} + \frac{V_a - V_b}{3} + \frac{V_a - V_c}{4} + 3 = 0$$

$$\Rightarrow \frac{12V_a - 60 + 4V_a - 4V_b + 3V_a - 3V_c + 108}{12} = 0$$

$$\Rightarrow 19V_a - 4V_b - 3V_c = -48$$

or,

$$\frac{V_b - V_a}{3} + \frac{V_b - V_c}{3} - \frac{6}{1} = 0$$

$$\Rightarrow \frac{V_b - V_a + V_b - V_c - 18}{3} = 0$$

$$\Rightarrow -V_a + 2V_b - V_c = 18$$

or

$$\frac{V_c - 10}{1} + \frac{V_c - V_b}{3} + \frac{V_c - V_a}{4} - \frac{3}{1} = 0$$

$$\Rightarrow \frac{12V_c - 120 + 4V_c - 4V_b + 3V_c - 3V_a - 108}{12} = 0$$

$$\Rightarrow -3V_A - 4V_B + 19V_C = 928$$

$$V_A \quad x = 4.22$$

$$V_B \quad y = 19.5$$

$$V_C \quad z = 16.77$$


$\therefore$ current across 4Ω resistance,

$$I = \frac{V_A - V_C}{4}$$

$$= \frac{4.22 - 16.77}{4}$$

$$\Rightarrow 3.2375 \text{ A}$$

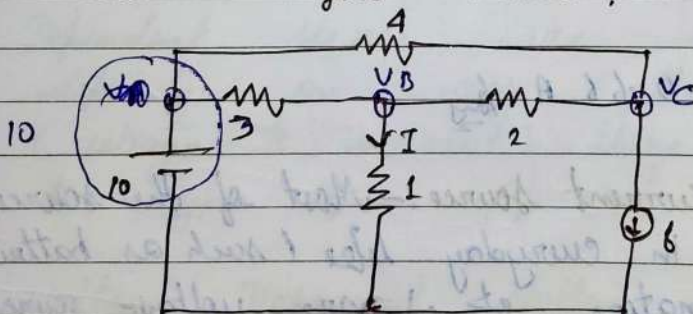Ques) find current across 1Ω resistance by using Nodal Analysis method?



Soln) $\frac{10 - V_A}{3} + \frac{10 - V_C}{4} \quad V_A = 10$

$$\frac{V_B - 10}{3} + \frac{V_B}{1} + \frac{V_B - V_C}{2} = 0 \quad \text{--- (I)}$$

$$\frac{V_C - V_B}{2} + \frac{V_C - 10}{4} + 6 = 0 \quad \text{--- (II)}$$

$$\text{from ①} \quad \frac{2V_b - 20 + 8V_b + 9V_b - 3V_c}{6} = 0$$

$$11V_b - 3V_c = 20 \quad \text{--- ①}$$

$$\text{from ②} \quad \frac{2V_c - 2V_b + V_c - 10 + 24}{4} = 0$$

$$\Rightarrow 3V_c - 2V_b + 14 = 0$$

$$V_b = 0.66 \text{ V} - 4.4 \text{ A}$$

$$V_c = -4.22 \text{ V} - 22.8$$

$$\therefore \text{Current} = \frac{V_b}{1} = \frac{0.66}{1} \text{ A} = 0.66 \text{ A}$$

$$= \frac{-4.4}{1} = -4.4 \text{ A}$$

$$V_b = 0.66$$

$$V_c = -4.22$$

$$\therefore I = 0.66 \text{ A}$$


★.) Voltage and current source:— Most of the source, encountered in everyday life (such as batteries, dynamos, alternators etc.) are voltage sources but some current sources do exist. Some Eg are:— Photoelectric cells as used in meters, metadyne generators as used in military gun controls. Other devices may be regarded as current sources, such as the collector circuits of transistors and the anode circuits pentode thermionic tubes. So, there are only two types of sources:— Current & Voltage source.

Imp.

★. Dependent OR Independent source :-

→ Independent source :-

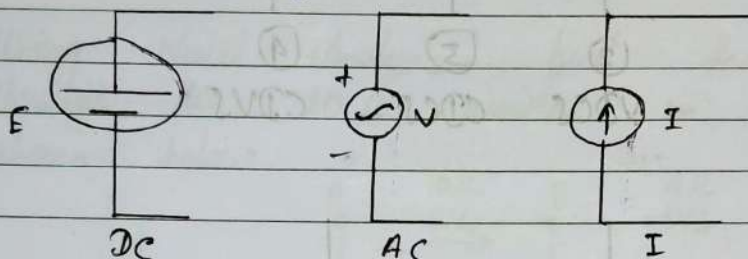A source is said to be independent when it does not depend on any other quantity in the ckt circuit




→ Dependent source :-


A dependent source is one which depends on some other quantity in ckt, which may be either a voltage or a current.

Dependent source are those source which depends on any other quantity (voltage & current) there are basically 4 types of dependent source :-

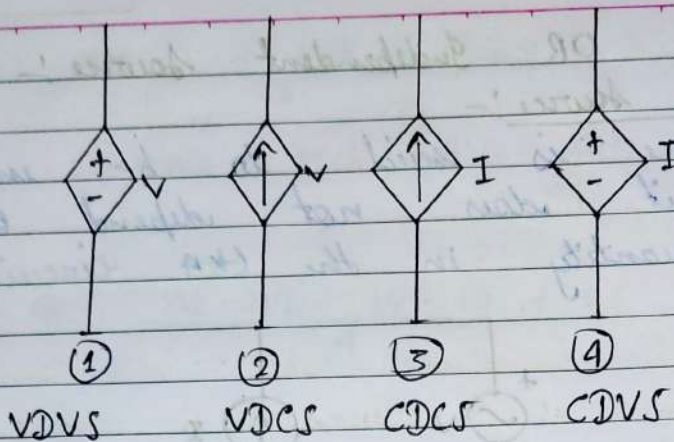- ① Voltage Dependent voltage source
- ② Voltage Dependent current source
- ③ Current Dependent current source
- ④ Current Dependent voltage source.




①

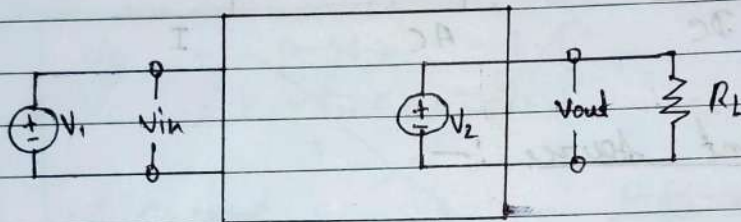


Voltage independent voltage source

②

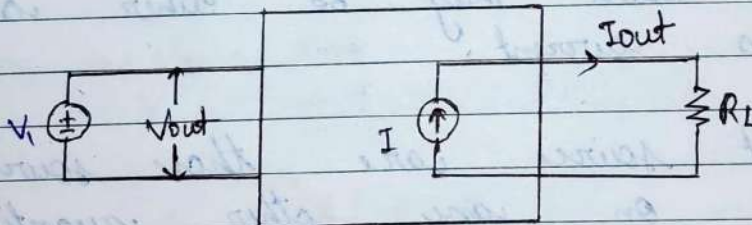


Voltage Dependent current source

③

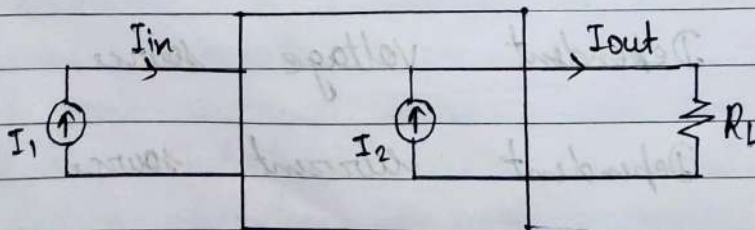

Current Dependent current source

(4)

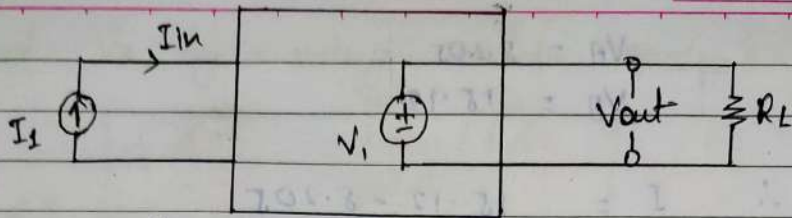


current independent voltage source.

Assignment - 1

(Q.)

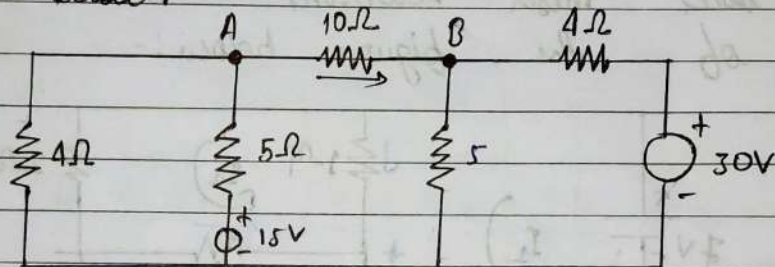Using Nodal Analysis, find the current through the 10Ω resistor in the figure shown below.



Solution

$$\frac{V_A}{4} + \frac{V_A - V_B}{10} + \frac{V_A - 15}{5} = 0$$

$$\Rightarrow \frac{5V_A + 2V_A - 2V_B + 4V_A - 60}{20} = 0$$

$$\Rightarrow 11V_A - 2V_B = 60 \quad \text{--- (1)}$$

✱

$$\frac{V_B - V_A}{10} + \frac{V_B - 30}{4} + \frac{V_B}{5} = 0$$

$$\Rightarrow \frac{2V_B - 2V_A + 5V_B - 150 + 4V_B}{20} = 0$$

$$\Rightarrow -2V_A + 11V_B - 150 = 0$$

$$\Rightarrow -2V_A + 11V_B = 150 \quad \text{--- (2)}$$


$$V_A = 8.205$$

$$V_D = 15.12$$

$$\therefore I = \frac{15.12 - 8.205}{10}$$

$$\Rightarrow 0.6915 \text{ A}$$

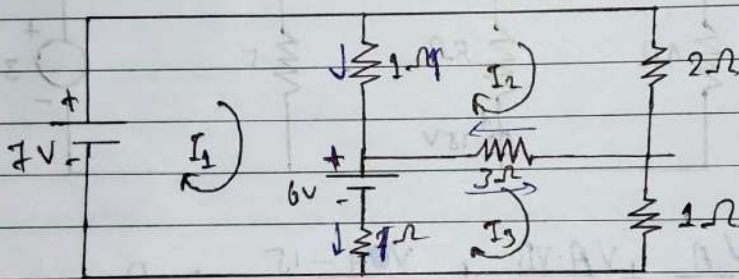Q. Use Mesh analysis to determine the three mesh current in the circuit of the figure below:-



Soln:

$$7 - (I_1 - I_2) - 6 - 2(I_1 - I_3) = 0$$

$$\Rightarrow 1 - I_1 + I_2 - 2I_1 + 2I_3 = 0$$

$$\Rightarrow -3I_1 + I_2 + 2I_3 = -1 \quad \text{--- (I)}$$

$$-3(I_2 - I_3) - 1(I_2 - I_1) - 2I_2 = 0$$

$$\Rightarrow 3I_2 + 3I_3 - I_2 + I_1 - 2I_2 = 0$$

$$\Rightarrow I_1 + 6I_2 + 3I_3 = 0 \quad \text{--- (II)}$$

$$-2(I_3 - I_1) + 6 - 3(I_3 - I_2) - I_3 = 0$$

$$\Rightarrow -2I_3 + 2I_1 + 6 - 3I_3 + 3I_2 - I_3 = 0$$


$$\Rightarrow 2I_1 + 3I_2 - 6I_3 = -6$$

$$I_1 = 0.5625 \text{ A}$$

$$I_2 = 0.5 \text{ A}$$

$$I_3 = 0.1875 \text{ A}$$

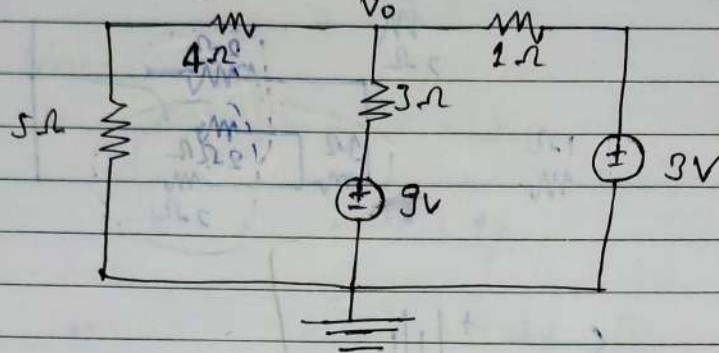Ques) find V_0 by using nodal analysis method?



Soln)

$$\frac{V_0}{9} + \frac{V_0 - 9}{3} + \frac{V_0 - 3}{1} = 0$$


$$\frac{V_0 + 3V_0 - 27 + 9V_0 - 27}{9} = 0$$

$$\Rightarrow 13V_0 - 54 = 0$$

$$\Rightarrow \therefore V_0 = \frac{54}{13}$$





$$V_0 \Rightarrow 4.15 \text{ V}$$

Ques)

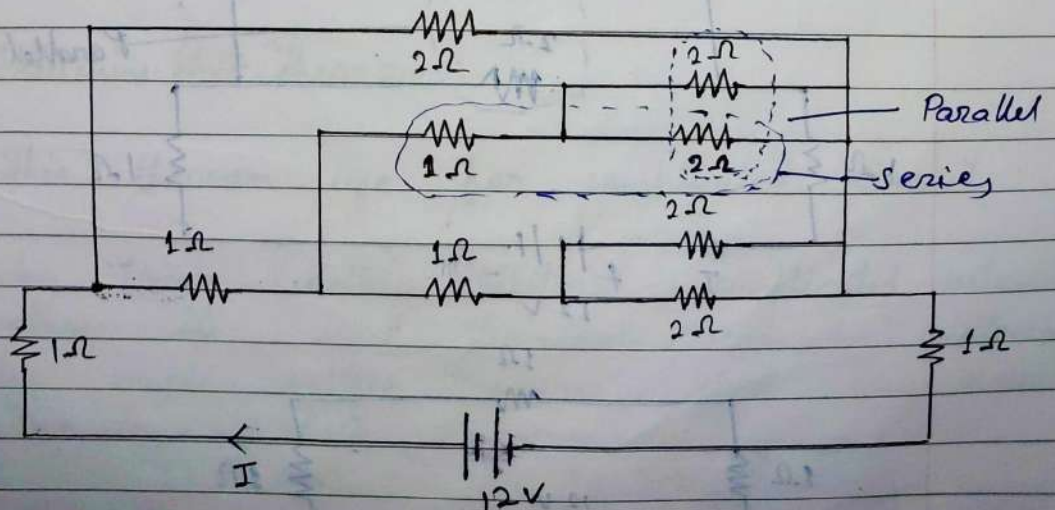

find the value of current 'I'.

Soln:

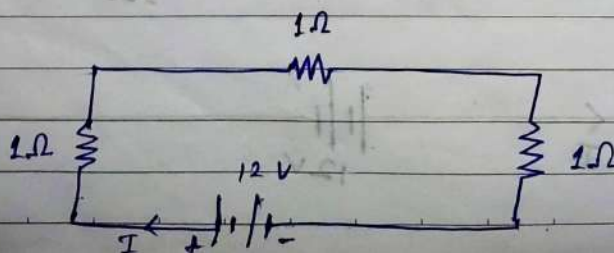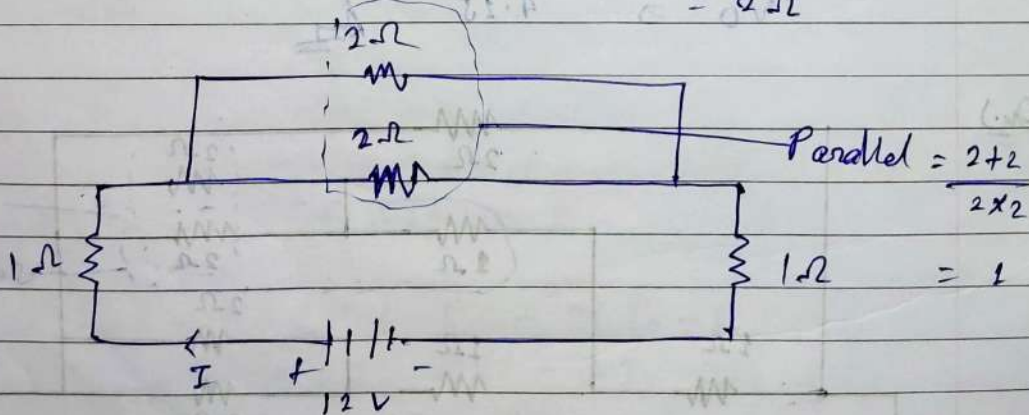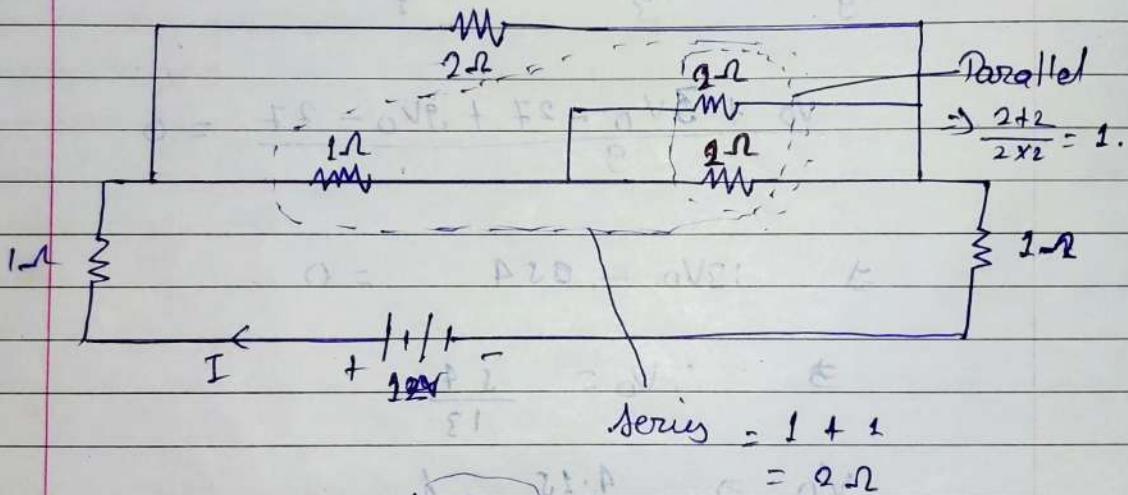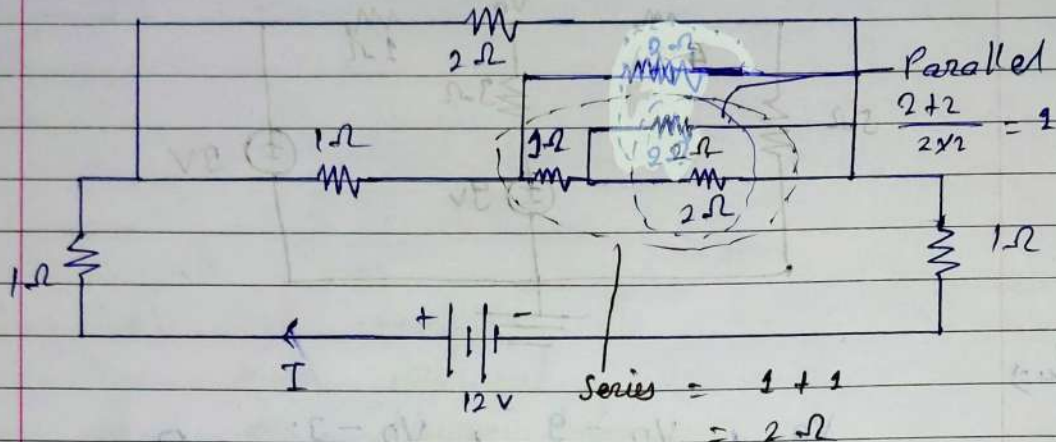


Now,

$$\text{current} = I = \frac{V}{R}$$

$$\Rightarrow \frac{12}{3}$$

$$\Rightarrow 4 \text{ Amp. } I_2$$

Voltage Division Rule :-

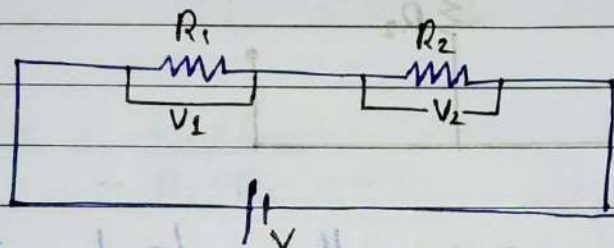

$$\therefore V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$\neq$


$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

Thevenin's Theorem :-


This theorem use for complicated circuit :

Any linear active bilateral complicated network across its load terminals can be replaced by single voltage source and one series resistance. (V_{th} , R_{th}).

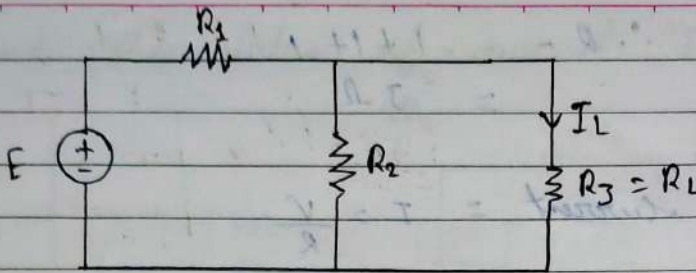
Step to apply thevenin's theorem / procedures :-



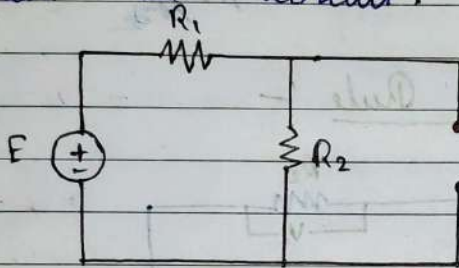
- i) first of all remove the load resistance from the circuit:-



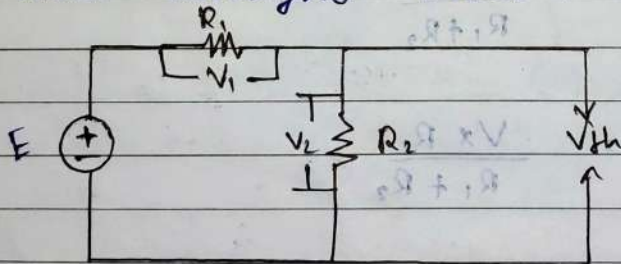- ii) find V_{th} across the load terminal by using voltage division rule / mesh method / Nodal analysis method.



Voltage division rule

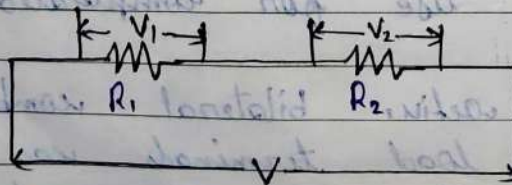


$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$


$$V_2 = V_{th} = \frac{E \times R_2}{R_1 + R_2} \quad (\text{by using voltage div rule}).$$

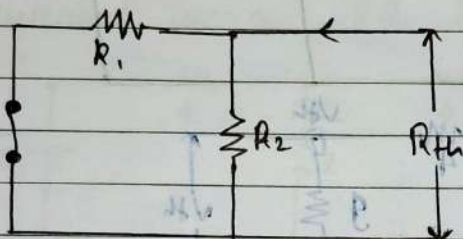- (iii.) find R_{th} across load terminal and short the voltage source or battery and open the current source.



$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2}$$

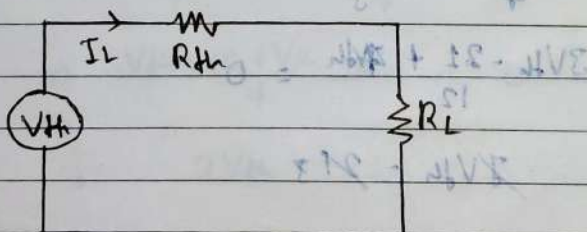- (iv.) Now draw the thevenins equivalent circuit and find I_L across load terminal.



$$\therefore I_L = \frac{V}{R} = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

where,


V_{th} = Thevenins equivalent voltage

R_{th} = Thevenins resistance


R_L = Load resistance

$I_L =$ Load current.

Ques) find current across 4Ω resistance

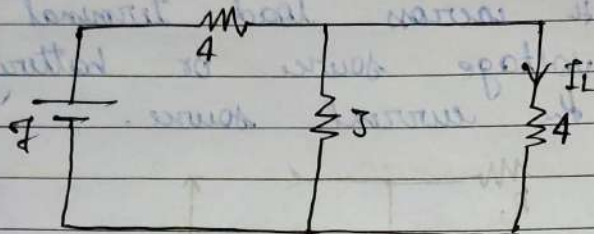

Solu. $\Rightarrow$

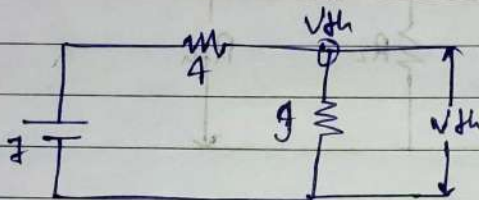


$$\therefore V_{th} = \frac{E \times R_2}{R_1 + R_2}$$

$$\frac{V_{th} - 7}{4} + \frac{V_{th}}{3} = 0$$

$$\Rightarrow \frac{3V_{th} - 21 + 4V_{th}}{12} = 0$$

$$\Rightarrow 7V_{th} = 21$$

$$\therefore V_{th} = 3$$

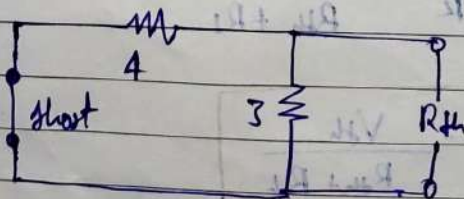


$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{4 \times 3}{4 + 3} = 1.71$$

Now, I_L across 4Ω resistance = $\frac{V_{th}}{R_{th} + R_L}$


$$= \frac{3}{1.71 + 1}$$

$$\Rightarrow 0.525$$

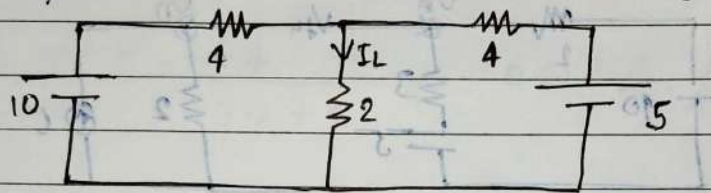Qn.) find current across 2Ω by using Thevenin's theorem?



Soln. $\Rightarrow$

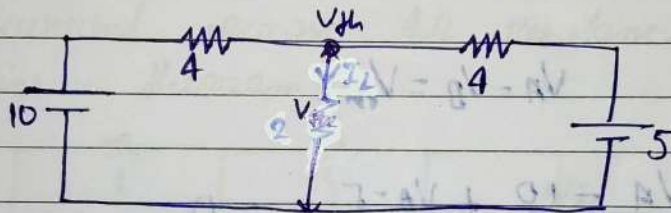


$$\frac{V_{th} - 10}{4} + \frac{V_{th} - 5}{4} = 0$$

$$\Rightarrow \frac{V_{th} - 10 + V_{th} - 5}{4} = 0$$


$$\Rightarrow 2V_{th} = 15$$

$$\therefore V_{th} = 7.5$$

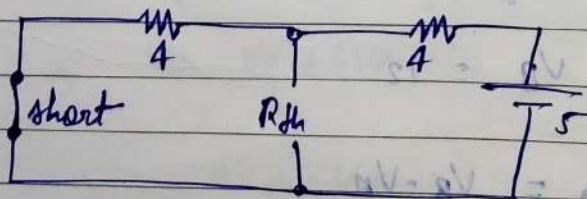


$$R_{th} = \frac{4 \times 4}{4 + 4} \Rightarrow 2$$

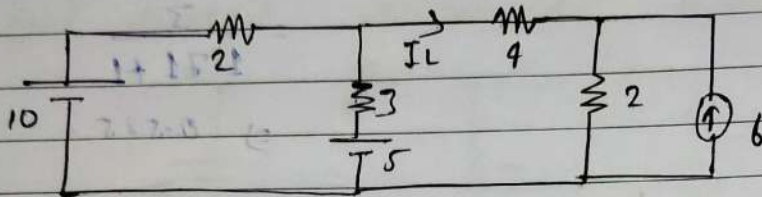Q.1) find current across 4Ω resistance using Thevenin's theorem?



Soln:

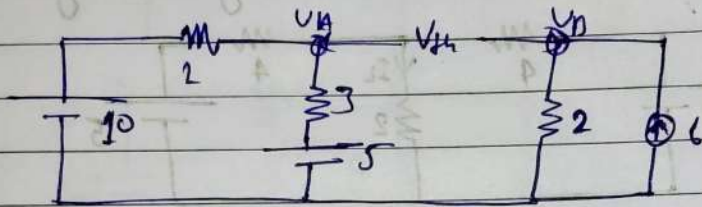

$$V_A - V_B = V_{th}$$

$$\frac{V_A - 10}{2} + \frac{V_A - 5}{3} = 0$$

$$\frac{3V_A - 30 + 2V_A - 10}{6} = 0$$

$$V_A = 8$$

✱

$$\frac{V_B}{2} + 6 = 0$$

$$\Rightarrow \frac{V_B + 12}{2} = 0$$


$$\Rightarrow V_B = -12$$

Now,

$$V_{th} = V_B - V_A$$

$$= -12 - 8$$


$$= -20$$

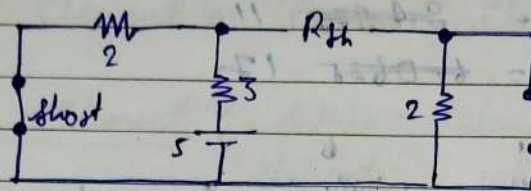


$$R_{th} = \frac{2 \times 3}{2 + 3} + 2 \Rightarrow \frac{6}{5} + 2 \Rightarrow 3.2 \Omega$$

$$\therefore I = \frac{4}{3.2 + 4} \Rightarrow 0.55 \text{ A. Ans}$$

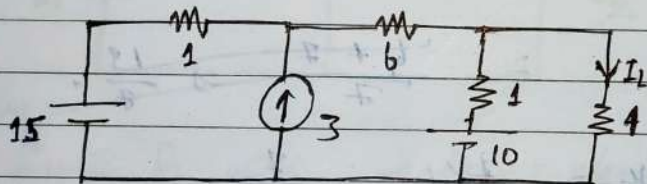Ques) find current across 4Ω resistance by using Thevenin's theorem?



Solu:-

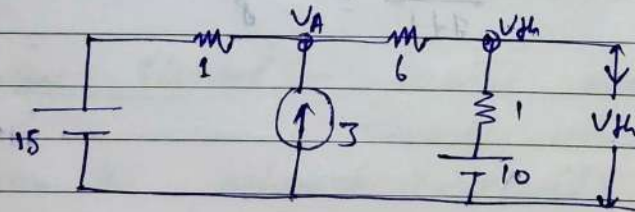

$$\frac{V_{th} - V_A}{6} + \frac{V_{th} - 10}{1} = 0$$

$$\Rightarrow \frac{V_{th} - V_A + 6V_{th} - 60}{6} = 0$$

$$\Rightarrow 7V_{th} - V_A = 60$$

≠

$$\frac{V_A - 15}{1} + \frac{V_A - V_{th}}{6} - 3 = 0$$


$$\Rightarrow 7V_A - V_{th} = 108 \quad \text{--- (2)}$$

$$6V_A - 90 + V_A - V_{th} - 18 = 0$$

$$7V_A - V_{th} - 108 = 0$$

$$V_{th} = \cancel{3.4975} \text{ V}$$

$$V_A = \cancel{6.0625} \text{ V}$$

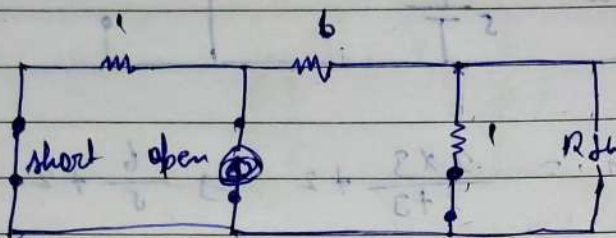

$$R_{th} = \frac{6 \times 1}{6 + 1}$$

$$= \frac{6}{7}$$

$$= \frac{6 + 7}{7} = \frac{13}{7}$$

$$R_{th} = \frac{7 \times 1}{7 + 1} = \frac{7}{8}$$

$$V = \frac{0.1 - 4V}{2} + \frac{4V - 4V}{2}$$

$$0 = 0.05 - 4V + 4V - 4V$$


$$0.05 = 4V - 4V$$

$$V = \frac{4V - 4V}{4} + \frac{4V - 4V}{4}$$

*.) Active Element or Passive Element

→ Active Elements: Active elements are those elements which supply energy to the network are called active element (current).

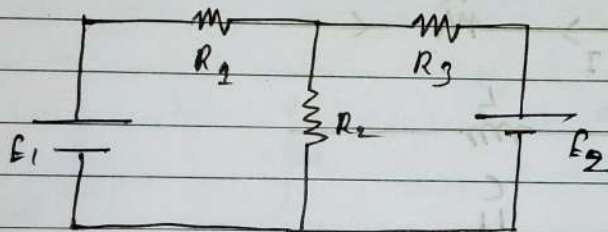Eg:- Voltage source and current source are active element




Here,

E_1 & E_2 are active element

→ Passive Element: Passive elements are those element which receive energy from the network (circuit) are called passive element.

for Eg:- Resistor, Inductor and capacitor are passive element.

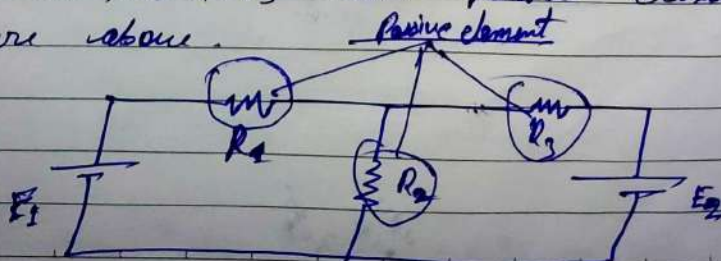
R_1 , R_2 & R_3 are passive element in the figure above.




★) Bilateral Element :-

Bilateral elements are those element whose properties and characteristics are the same in either direction.

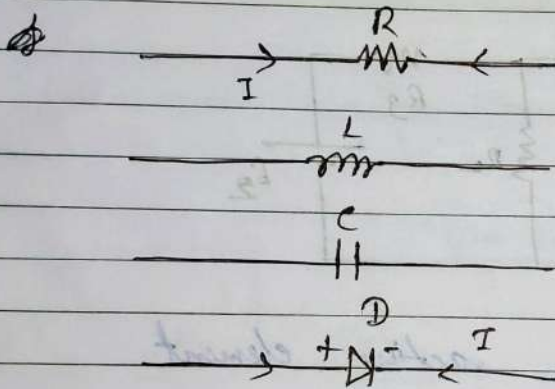
for eg :- Resistor, Inductor and capacitor are bilateral elements and diodes are unidirectional device.




★) Source Conversion Method :-

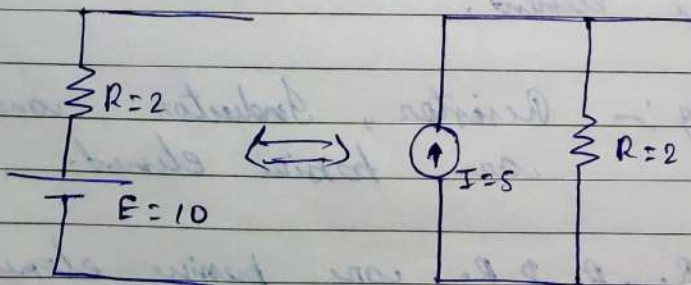

Q.2)

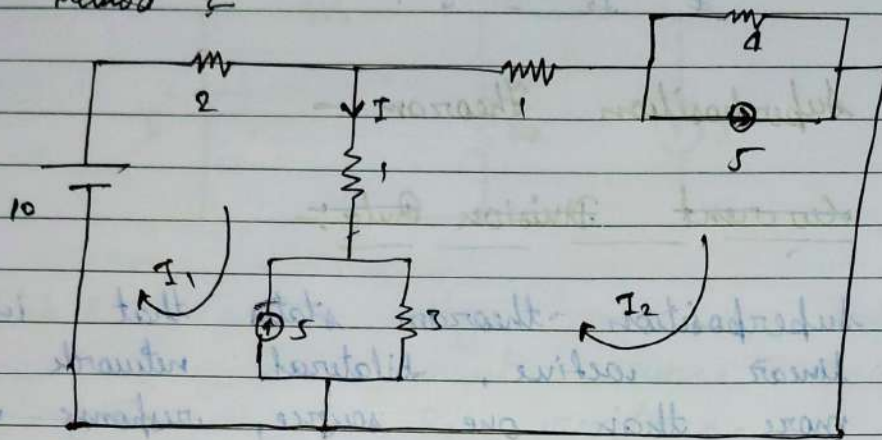find I_1 & I_2 by using Mesh Analysis method?

soln

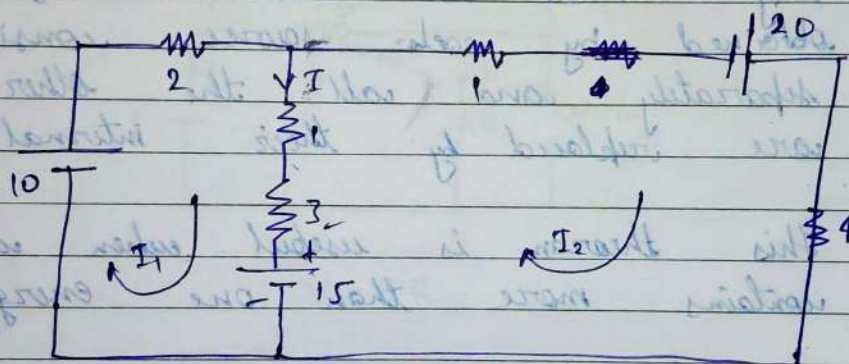

$$10 - 2I_1 - 4(I_1 - I_2) - 15 = 0$$

$$\Rightarrow 10 - 2I_1 - 4I_1 + 4I_2 - 15 = 0$$

$$\Rightarrow -6I_1 + 4I_2 = 5 \quad \text{--- (1)}$$

$$15 - 4(I_2 - I_1) - 1(I_2) + 20 - 4I_2 = 0$$

$$\Rightarrow 15 - 4I_2 + 4I_1 - I_2 + 20 - 4I_2 = 0$$

$$\Rightarrow 35 - 5I_2 + 4I_1 - 4I_2 = 0$$

$$4I_1 - 9I_2 = -35 \quad \text{--- (2)}$$


$$\therefore I_1 = 2.5$$

$$\& I_2 = 5$$

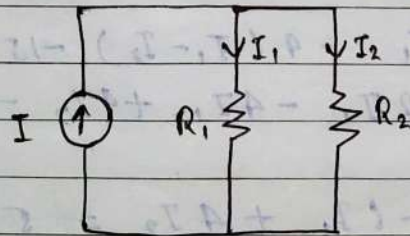* 1) Superposition Theorem :-

Current Division Rule :-


- ① Superposition theorem states that in any linear active, bilateral network having more than one source, response across any elements is the sum of responses obtained by each source consider ~~to~~ separately and all the other source are replaced by their internal resistance.
- ② This theorem is useful when a network contains more than one energy source.
- ③ Current Division Rule :-




$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$I_2 = \frac{I R_1}{R_1 + R_2}$$

Procedure :-

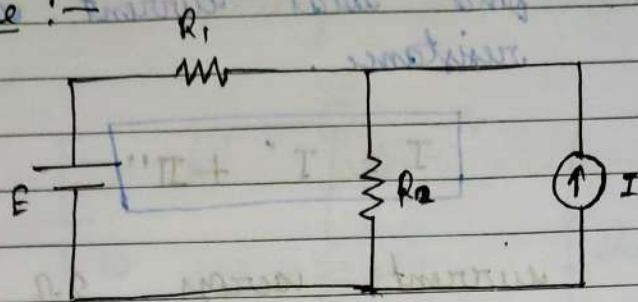


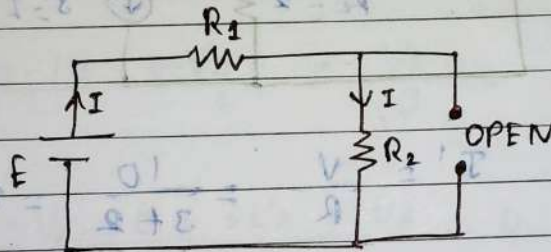Step 1:- Consider voltage source or battery and open the current source and find I across R_2 resistance.



$$\Rightarrow I = \frac{E}{R_1 + R_2} \quad \text{--- (1)}$$

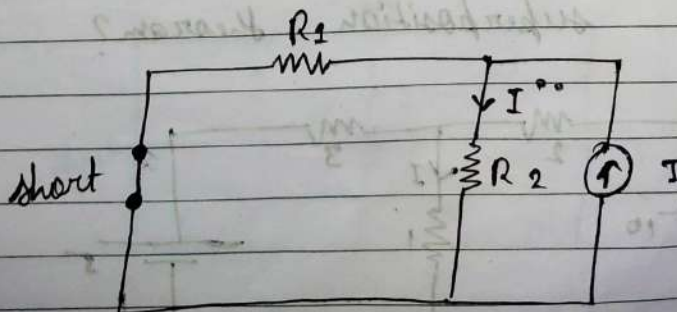Step 2:- Consider current source and short the voltage source or battery and find ' I ' across R_2 resistance.




$$I'' = I \times R \quad \text{--- (2)}$$

Step 3:- find total current across R_2 resistance.

$$I = I' + I''$$

Qn.1) find current across 2Ω resistance by using superposition method / theorem?

Solu. →

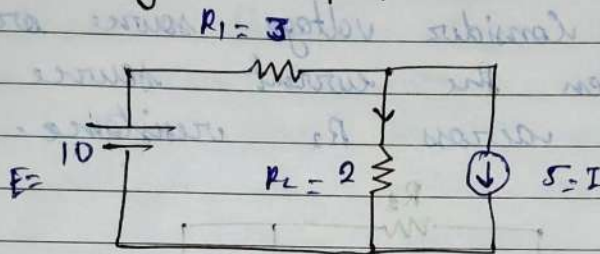

Solu. →

$$I' = \frac{V}{R} = \frac{10}{3+2} = 2$$


$$I'' = \frac{5 \times R_1}{R_1 + R_2} = \frac{5 \times 3}{3+2} = 3$$

$$\therefore I = I' + I''$$

$$= 2 + 3$$

$$= 5$$

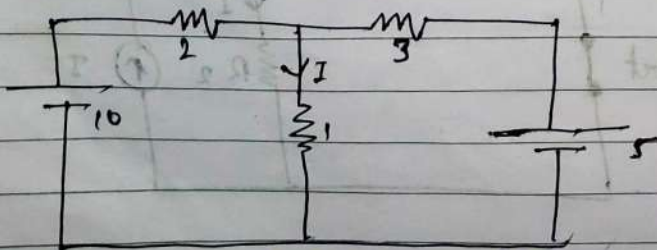
Qn.2) find current across 1Ω resistance by using superposition theorem?



Step - I

Soln:

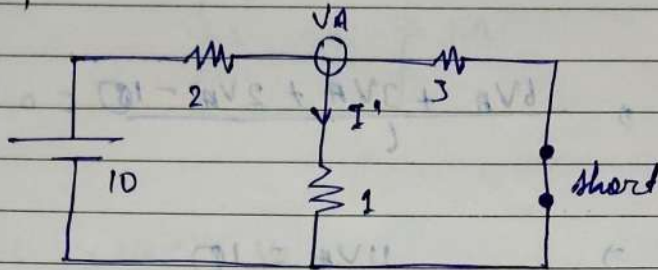Consider 10 V battery and short the other source,



$$I' = \frac{V_A}{1}$$

$$\frac{V_A - 10}{2} + \frac{V_A}{1} + \frac{V_A}{3} = 0$$


$$\Rightarrow \frac{3V_A - 20 + 6V_A + 2V_A}{6} = 0$$

$$\Rightarrow 11V_A = 20$$

$$\therefore V_A = 2.72 = I'$$

Step II:-

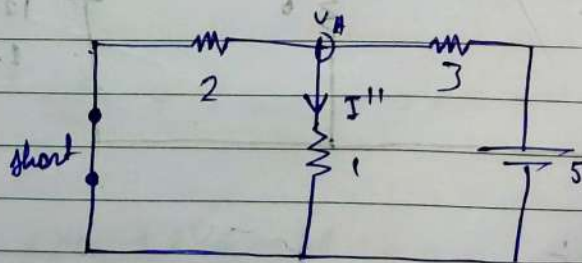Consider 5 V battery and short the other source,



$$I'' = \frac{V_A}{1}$$

$$\frac{V_A}{1} + \frac{V_A}{2} + \frac{V_A - 5}{3} = 0$$

$$\Rightarrow \frac{6V_A + 3V_A + 2V_A - 10}{6} = 0$$

$$\Rightarrow 11V_A = 10$$

$$\therefore V_A = \frac{10}{11}$$


$$\therefore I'' = 0.90$$

$$\therefore I_2 = I' + I''$$

$$= 2.72 + 0.90$$


$$= 3.62 \text{ A}$$

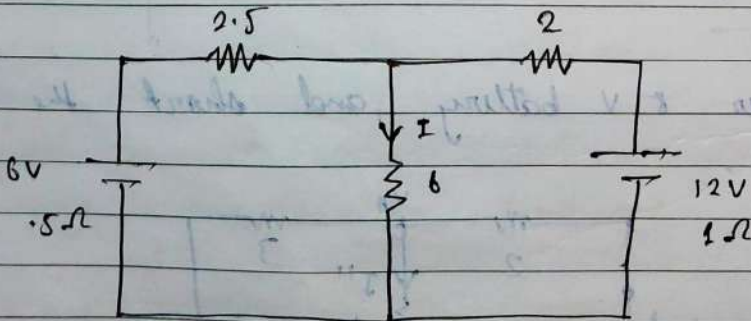Ques: find current across 6Ω resistance using superposition method?



Soln: Step 1:-

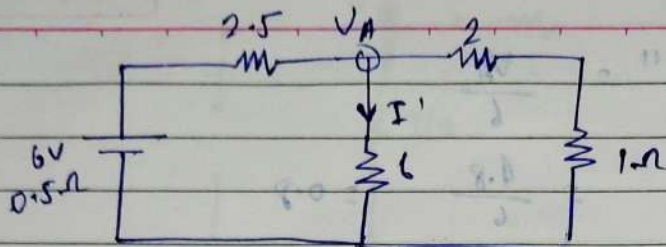Replace the source by their internal resistance.



$$\frac{V_A - 6}{3} + \frac{V_A}{6} + \frac{V_A}{3} = 0$$


$$\Rightarrow \frac{2V_A - 12 + V_A + 2V_A}{6} = 0$$

$$\Rightarrow 5V_A = 12$$

$$\therefore V_A = \frac{12}{5} = 2.4 \text{ V}$$

$$\therefore I' = \frac{V_A}{6} = \frac{12}{5 \times 6} = 0.4 \text{ A}$$

2

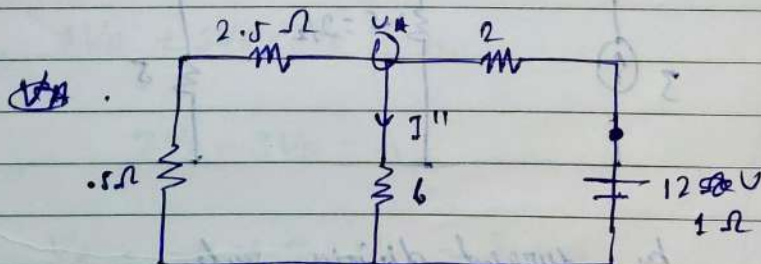

$$\frac{V_A}{3} + \frac{V_A}{6} + \frac{V_A - 12}{3} = 0$$

$$\frac{2V_A + V_A + 2V_A - 24}{6} = 0$$

$$V_A = \frac{24}{5} = 4.8 \text{ V}$$

$$\therefore I'' = \frac{V_A}{6}$$

$$= \frac{4.8}{6} = 0.8$$


$$\therefore I^{\oplus} = I' + I''$$

$$= 0.4 + 0.8$$

$$I = 1.2 \text{ A}$$

Ques) find the value of circuit in branch A B or find current across A B by using superposition theorem?

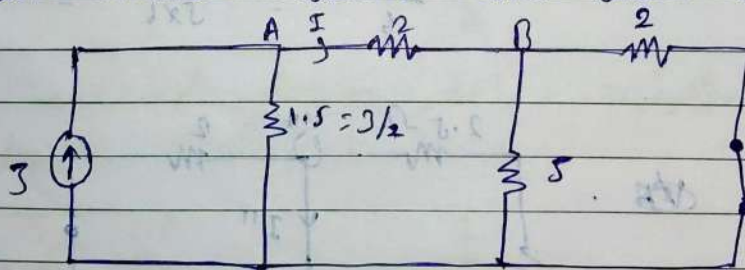
Soln) Consider current source and short the battery.



by current division rule,

$$I' = \frac{3 \times \frac{3}{2}}{\frac{3}{2} + 2}$$

$$I = 1.29 \text{ A}$$

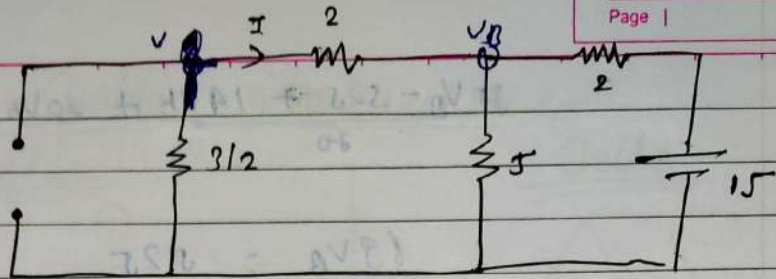

Nodal Analysis method,
by using ~~current division rule~~

$$\frac{V_A - 15}{2} + \frac{V_B}{5} + \frac{V_B - V_A}{2} = 0$$

$$\Rightarrow \frac{5V_B - 75 + 2V_B + 5V_B - 5V_A}{10} = 0$$

$$\Rightarrow -5V_A + 12V_B = 75 \quad \text{--- (1)}$$

✱

$$\frac{2V_A}{3} + \frac{V_A - V_B}{2} = 0$$

$$\Rightarrow \frac{4V_A + 3V_A - 3V_B}{6} = 0$$

$$\Rightarrow 7V_A - 3V_B = 0$$

$$V_A = 3.26 \text{ V} \quad V_B = 7.6 \text{ A}$$

$$\therefore I = \frac{V_B - V_A}{2}$$

$$\frac{V_B - 15}{2} + \frac{V_B}{5} + \frac{V_B}{3/2 + 2}$$

$$\Rightarrow \frac{V_B - 15}{2} + \frac{V_B}{5} + \frac{2V_B}{7}$$

$$\frac{35V_0 - 525 + 14V_0 + 20V_0}{70} = 0$$

$$69V_0 = 525$$

$$\therefore V_0 = \frac{525}{69} = 7.60$$

$$I'' = \frac{V_0}{2} = \frac{7.60}{2} = 3.8A$$

$$\begin{aligned} \therefore I &= I' - I'' \\ &= 3.8 - 1.29 \\ &= 2.51A \end{aligned}$$

$$(1) \quad 25 = 10V_1 + 5V_2$$

$$25 = \frac{10V_1 + 5V_2}{5} \quad \cdot \quad \frac{10V_1}{5}$$

$$25 = 2V_1 + V_2 + 10V_1$$

$$25 = 12V_1 + V_2$$


$$12.5 = 6V_1 + 0.5V_2$$

$$\frac{12.5 - 6V_1}{0.5} = 12.5 - 12V_1$$

$$\frac{12.5}{0.5} - \frac{6V_1}{0.5} = 12.5 - 12V_1$$

$$\frac{12.5}{0.5} - \frac{6V_1}{0.5} = 12.5 - 12V_1$$


★) Star - Delta conversion !

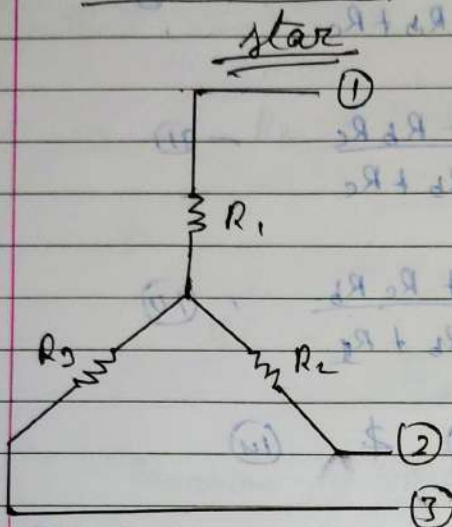

$$R_{12} = R_1 + R_2$$

$$R_{13} = R_1 + R_3$$

$$R_{23} = R_2 + R_3$$

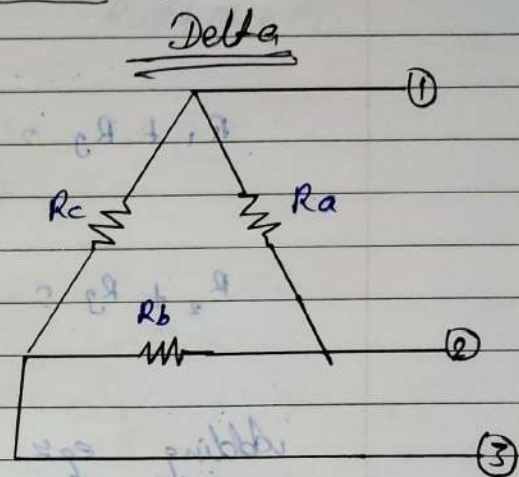

$$R_{12} = \frac{(R_c + R_b) \times R_a}{R_a + R_b + R_c}$$

$$R_{13} = \frac{(R_a + R_b) \times R_c}{R_a + R_b + R_c}$$

$$R_{23} = \frac{(R_a + R_c) \times R_b}{R_a + R_b + R_c}$$

$$R_{12} = \frac{R_a R_c + R_a R_b}{R_a + R_b + R_c}$$

$$R_{13} = \frac{R_a R_c + R_b R_c}{R_a + R_b + R_c}$$

$$R_{23} = \frac{R_a R_b + R_c R_b}{R_a + R_b + R_c}$$

Now,

On comparing,



Date |

Page |

$$R_1 + R_2 = \frac{R_a R_c + R_a R_b}{R_a + R_b + R_c} \quad \text{--- (I)}$$

$$R_1 + R_3 = \frac{R_a R_c + R_b R_c}{R_a + R_b + R_c} \quad \text{--- (II)}$$

$$R_2 + R_3 = \frac{R_a R_b + R_c R_b}{R_a + R_b + R_c} \quad \text{--- (III)}$$

Adding eqs (I), (II) & (III)

$$R_1 + R_2 + R_1 + R_3 + R_2 + R_3 = R_a R_c + R_a R_b + R_a R_c + R_b R_c + R_a R_b + R_c R_b$$
$$2R_1 + 2R_2 + 2R_3 = \frac{2R_a R_c + 2R_a R_b + 2R_b R_c}{R_a + R_b + R_c}$$

$$\Rightarrow 2(R_1 + R_2 + R_3) = \frac{2(R_a R_c + R_a R_b + R_b R_c)}{R_a + R_b + R_c}$$

$$\Rightarrow R_1 + R_2 + R_3 = \frac{R_a R_c + R_a R_b + R_b R_c}{R_a + R_b + R_c} \quad \text{--- (IV)}$$

Subtracting eq (IV) by (I), eq (IV) by (II)
& eq (IV) by (III)

$$R_1 + R_2 + R_3 - R_1 + R_2 = \frac{R_a R_c + R_a R_b + R_b R_c}{R_a + R_b + R_c} - \frac{R_a R_c + R_a R_b}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c} \quad \text{--- (V)}$$

$$R_1 + R_2 + R_3 = R_1 + R_2 + R_3 = \frac{R_a R_c + R_a R_b + R_b R_c}{R_a + R_b + R_c} - R_a R_c - R_b R_c$$

$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c} \quad \text{--- (VI)}$$

≠

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c} \quad \text{--- (VII)}$$

Equations (V) (VI) & (VII) are star Delta to star.

Now,

Mul eqⁿ (V) x (6)

$$R_1 R_2 = \frac{R_b R_c}{R_a + R_b + R_c} \times \frac{R_a R_b}{R_a + R_b + R_c}$$

$$\Rightarrow \frac{R_a R_b^2 R_c}{(R_a + R_b + R_c)^2}$$

Mul eqⁿ (V) by (7)

$$R_1 R_2 \Rightarrow \frac{R_c^2 R_a R_b}{(R_a + R_b + R_c)^2}$$

≠

Mul eqⁿ (6) by (7)

$$R_1 R_2 \Rightarrow \frac{R_a^2 R_b R_c}{(R_a + R_b + R_c)^2}$$

Now,

Adding ,

$$R_2 R_3 + R_1 R_3 + R_1 R_2 = \frac{R_a R_b R_c (R_b + R_c + R_a)}{3 (R_a + R_b + R_c)^2}$$

$$R_2 R_3 + R_1 R_3 + R_1 R_2 = \frac{R_a R_b R_c}{R_a + R_b + R_c} \quad \text{--- (VIII)}$$

Now, Dividing eqⁿ (VIII) by (V)

$$\frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_3} = R_a \quad \text{--- (IX)}$$

Dividing eqⁿ (VIII) by (VI),

$$\frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_2} = R_c \quad \text{--- (X)}$$


Dividing eqⁿ (VIII) by (VII),

$$\frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1} = R_b \quad \text{--- (XI)}$$

This is the star Delta conversion.

Qⁿ find current across 2Ω or 1 by using

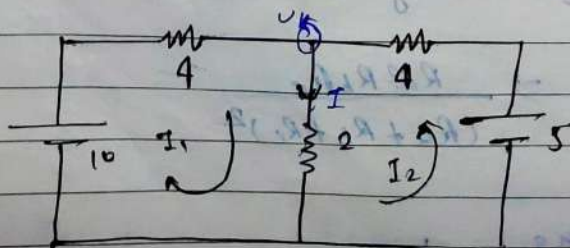- i.) Mesh analysis method
- ii.) Nodal
- iii.) Thevenin's theorem
- iv.) Superposition theorem.



Sol: i) Mesh Analysis Method,

$$10 - 4I_1 - 2(I_1 + I_2) = 0 \quad \text{--- (1)}$$

$$5 - 4I_2 - 2(I_2 - I_1) = 0 \quad \text{--- (2)}$$

from (1)

$$10 - 4I_1 - 2I_1 + 2I_2 = 0$$

$$-6I_1 + 2I_2 = -10$$

from (2)

$$5 - 4I_2 - 2I_2 + 2I_1 = 0$$

$$5 - 6I_2 - 2I_1 = 0$$

$$-2I_1 - 6I_2 = -5$$

$$I_1 (x) = 1.5625$$

$$I_2 (y) = 0.3125$$

$$I = I_1 + I_2$$

$$I = 2.00 \text{ A} \quad 1.875 \text{ A}$$

ii) Nodal Analysis Method,

$$\frac{V_A - 10}{4} + \frac{V_A}{2} + \frac{V_A - 5}{4} = 0$$


$$\frac{V_A - 10 + 2V_A + V_A - 5}{4} = 0$$

$$3 \quad 4V_A - 15 = 0$$

$$\therefore V_A = \frac{+15}{4} = +3.75$$

$$\therefore I = \frac{V_A}{2} = \frac{3.75}{2} = 1.875 \text{ A}$$

(iii) Thevenin's theorem,

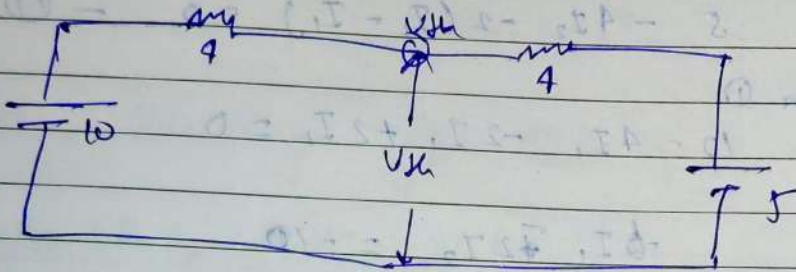


$$\frac{V_{th} - 10}{4} + \frac{V_{th} - 5}{4} = 0$$

$$\frac{V_{th} - 10 + V_{th} - 5}{4} = 0$$

$$2V_{th} = 15$$

$$\therefore V_{th} = 7.5$$

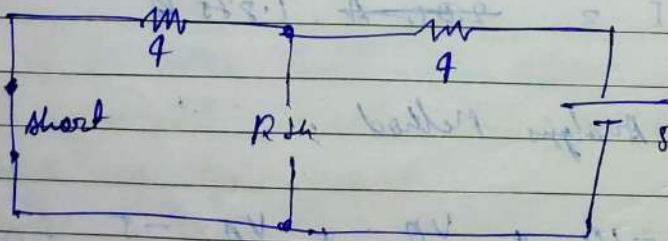


$$R_{th} = R_1 \parallel R_2$$

$$R_{th} = \frac{4 \times 4}{4 + 4} = 2$$

$$\therefore I = \frac{7.5}{2 + 2} = 1.875 \text{ A}$$

(12) Superposition theorem;

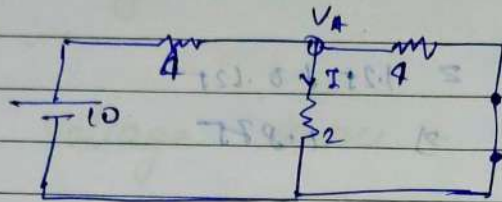


$$\frac{V_A - 10}{4} + \frac{V_A}{2} + \frac{V_A}{4} = 0$$

$$\Rightarrow \frac{V_A - 10 + 2V_A + V_A}{4} = 0$$

$$\Rightarrow 4V_A = 10$$

$$\Rightarrow \therefore V_A = 2.5$$
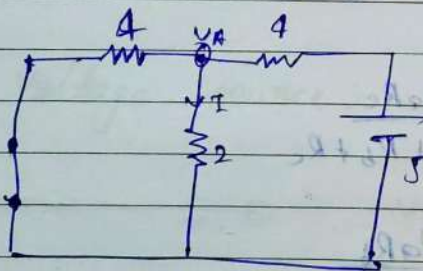
$$I' = \frac{V_A}{2} \Rightarrow \frac{2.5}{2} = 1.25$$



$$\frac{V_A}{2} + \frac{V_A}{4} + \frac{V_A - 5}{4} = 0$$

$$\Rightarrow \frac{2V_A + V_A + V_A - 5}{4} = 0$$

$$\Rightarrow 4V_A = 5$$


$$\therefore V_A = 1.25$$

$$\Rightarrow 0.625$$

$$I = I'' - I'$$

$$= 1.25 + 0.625$$

$$\Rightarrow 1.875$$

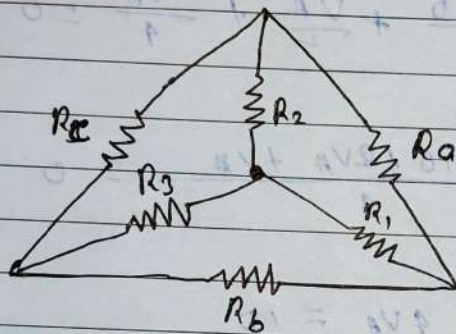

Delta to star:

$$R_g = \frac{R_c \times R_b}{R_a + R_b + R_c}$$

$$R_g = \frac{R_c R_c}{R_a + R_b + R_c}$$

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_b}$$


Star to delta

$$R_a = R_1 + R_2 + \frac{R_1 R_2}{R_g} \quad R_c = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

$$R_b = R_3 + R_2 + \frac{R_3 R_2}{R_1}$$


* Ideal Voltage source and Practical Voltage source :-

→ Ideal Voltage source :-

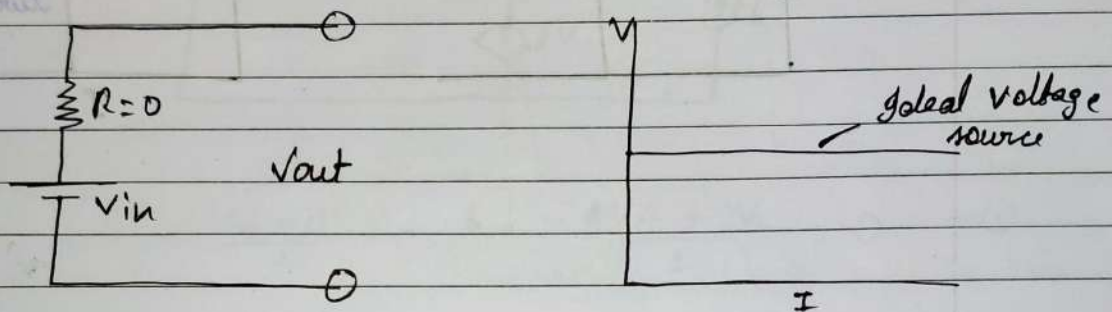

($V_{in} = V_{out}$) $R=0$ always


→ Practical Voltage source :-

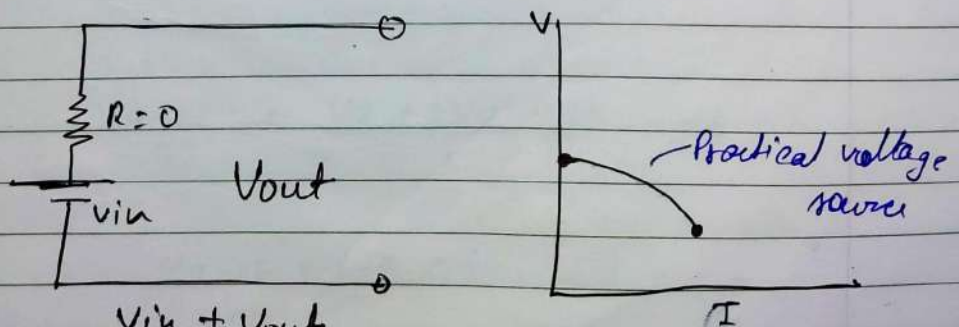


$V_{in} \neq V_{out}$

V_{in} is always greater than V_{out}

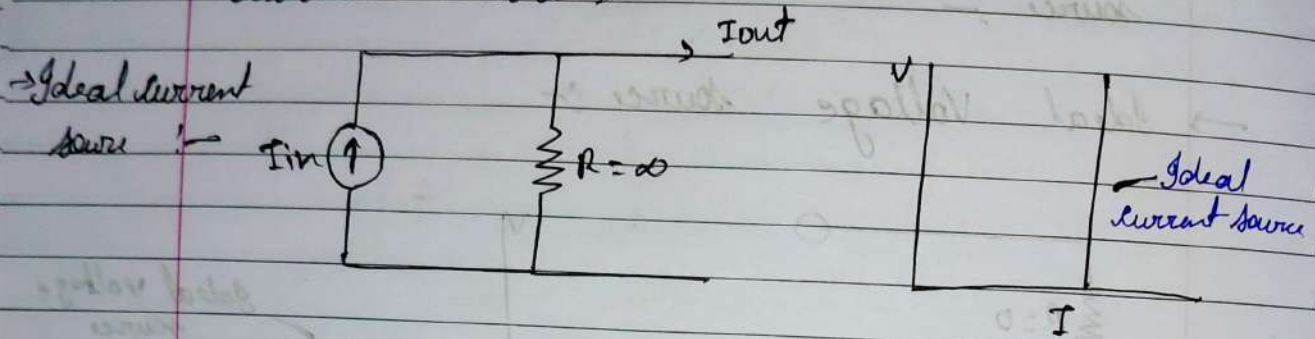
A.) Ideal current source and practical current source :-



Practical current source :-

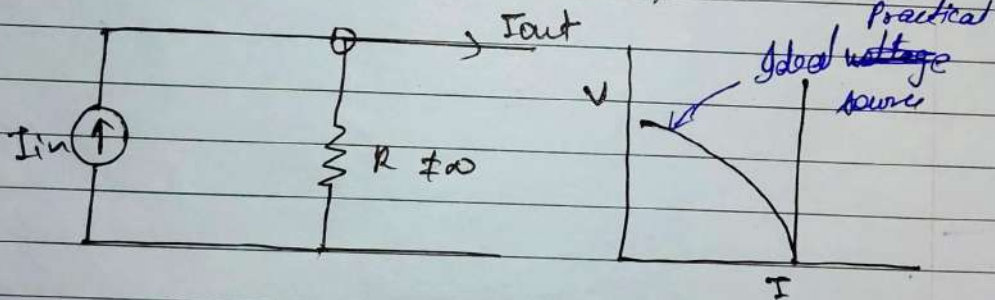

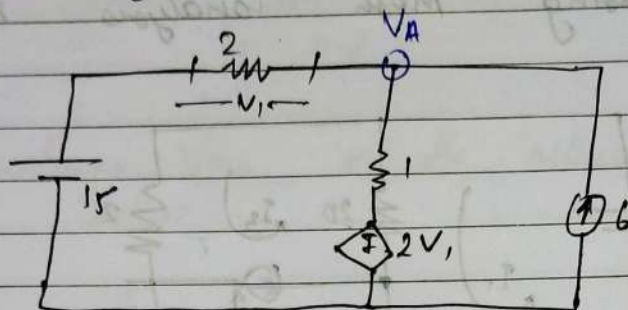Ques find V_s by using Nodal Analysis method?



Soln:

$$\frac{V_A - 15}{2} - 6 - \frac{V_A + 2V_1}{1} = 0 \quad \text{--- (1)}$$

$$\therefore V_1 = I \times 2$$

$$\therefore V_1 = -\frac{V_A - 15}{2} \times 2$$

$$V_1 = V_A - 15 = -I + 6$$

Put the value in eqn (1)

$$\frac{V_A - 15}{2} + \frac{V_A + 2(V_A - 15)}{1} - 6 = 0$$


$$\frac{V_A - 15}{2} + \frac{V_A + 2V_A - 30}{1} - 6 = 0$$

$$\frac{V_A - 15 + 6V_A - 60}{2} - 12 = 0$$

$$7V_A - 87 = 0$$

$$\therefore V_A = \frac{87}{7} = 12.42 \text{ volts}$$

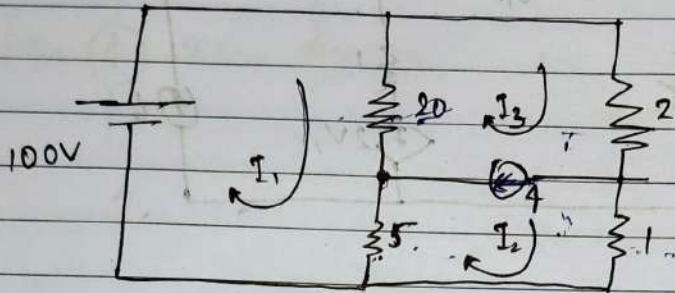Q.1) find current across 5Ω resistance by using mesh analysis method?



Soln

Super Mesh:-

$$4 + I_3 - I_2 = 0$$

$$100 - 20(I_1 - I_3) - 5(I_1 - I_2) = 0 \quad \text{--- (i)}$$

$$-5(I_2 - I_1) - 20(I_3 - I_1) - 2I_3 - I_2 = 0 \quad \text{--- (ii)}$$

$$4 + I_3 = I_2$$

$$I_2 - I_3 = 4$$

$$0I_1 + I_2 - I_3 = 4 \quad \text{--- (iii)}$$

from (i)

$$100 - 20I_1 + 20I_3 - 5I_1 + 5I_2 = 0$$

$$\Rightarrow 100 - 25I_1 + 5I_2 + 20I_3 = 0$$

$$\Rightarrow -25I_1 + 5I_2 + 20I_3 = -100$$

from (ii)

$$-5I_2 + 5I_1 - 20I_3 + 20I_1 - 2I_3 - I_2 = 0$$

$$\Rightarrow 25I_1 - 6I_2 - 22I_3 = 0$$

$$I_1 = 96.8$$

$$I_2 = 96$$

$$I_3 = 92$$

$$\begin{aligned} \therefore I &= I_1 - I_2 \\ &= 36.8 - 36 \\ &= 0.8 \end{aligned}$$

Ans 2

find voltage V_{ab} in the network shown below?


$$V = IR$$

$$30 = \frac{V}{4}$$

$$= \frac{30}{4}$$

$$= 7.5$$

$$= 3 \times 4 = 12$$

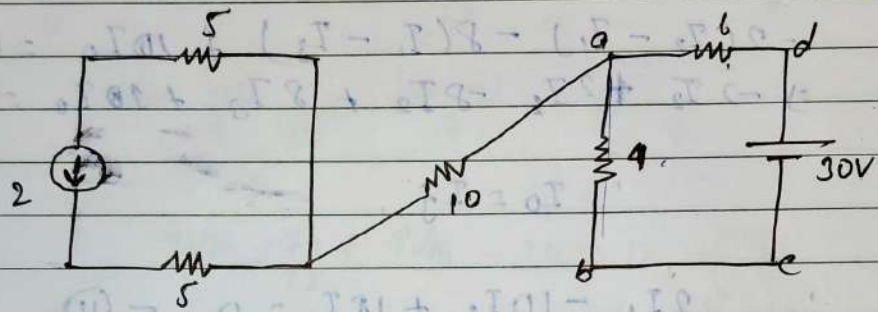

Soln

$$V_{ab} = IR$$


$$V_{ab} = I \times 4 \quad \text{--- (1)}$$

$$\therefore I = \frac{V}{R} = \frac{30}{10} = 3 \text{ A}$$

Put the value in eqⁿ (1).

$$\begin{aligned} V_{ab} &= 3 \times 4 \\ &= 12 \text{ V.} \end{aligned}$$

Ans

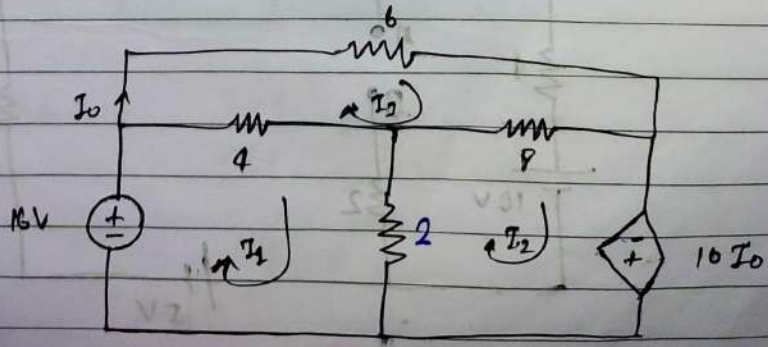

Using mesh analysis method find I_0 in the circuit is given above?

Soln

$$16 - 4(I_2 - I_3) - 2(I_1 - I_2) = 0$$

$$16 - 4I_1 + 4I_3 - 2I_1 + 2I_2 = 0$$

$$\Rightarrow -6I_1 + 2I_2 + 4I_3 = -16 \quad \text{--- (I)}$$

or

$$-2(I_2 - I_1) - 8(I_2 - I_3) + 10I_0 = 0$$

$$\Rightarrow -2I_2 + 2I_1 - 8I_2 + 8I_3 + 10I_0 = 0$$

$$\therefore I_0 = I_3$$

$$\therefore 2I_1 - 10I_2 + 18I_3 = 0 \quad \text{--- (II)}$$

$\neq$


$$-4(I_3 - I_1) - 6I_3 - 8(I_3 - I_2) = 0$$

$$\Rightarrow 4I_1 + 8I_2 - 18I_3 = 0 \quad \text{--- (III)}$$

$$I_1 = -2.57 \text{ A}, I_2 = -7.71 \text{ A} \neq I_3 = I_0 = -4 \text{ A}$$

Ans

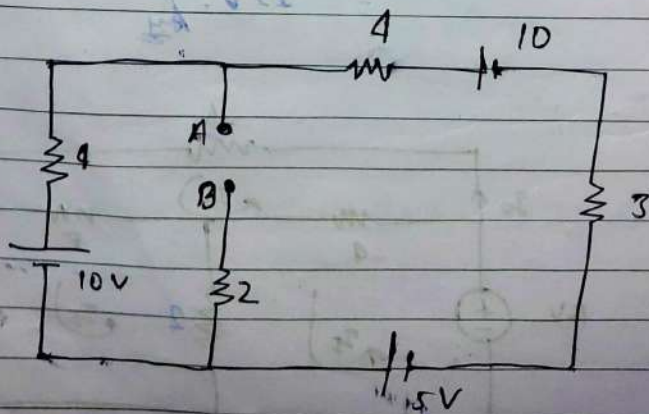find power in 8Ω resistor by Thevenin's theorem connected across AB?




$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Date |

Page |

Soln:

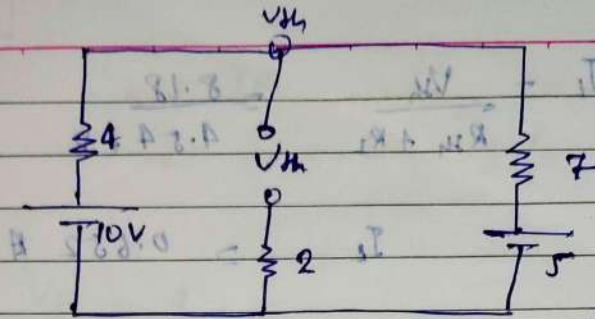

By using ~~Nodal~~ Nodal analysis method

$$\frac{V_{th} - 10}{4} + \frac{V_{th} - 5}{7} = 0$$


$$\Rightarrow \frac{7V_{th} - 70 + 4V_{th} - 20}{28} = 0$$

$$\Rightarrow \frac{11V_{th} - 90}{28} = 0$$

$$V_{th} = 8.18$$

≠

$R_{th} =$

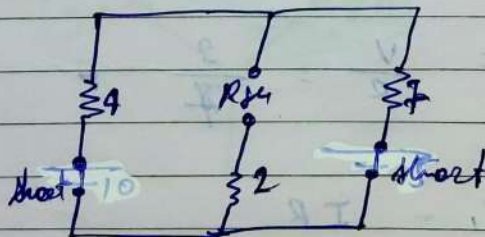

$$R_{th} = \frac{7 \times 4}{7 + 4} + 2$$

$$= 4.54$$

$$I_1 = \frac{V_{th}}{R_{th} + R_L} = \frac{8.18}{4.54 \text{ } \Omega}$$


$$I_L = 1.8 \text{ A}$$

$$\therefore P = I_L^2 R$$

$$= (0.652)^2 \times 8$$

$$P = 3.4 \text{ Watt}$$

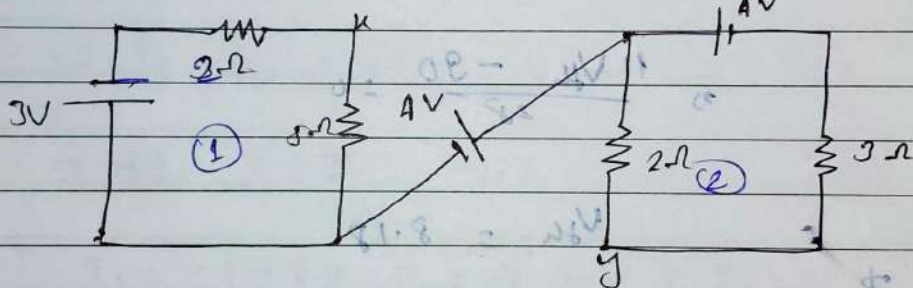Qn.) Calculate potential difference b/w x and y



Soln.) Voltage across 5Ω at 1st loop,

$$I = \frac{V}{R} = \frac{3}{7}$$

$$\therefore V_1 = IR$$

$$\rightarrow V_1 = \frac{3}{7} \times 5 = \frac{15}{7}$$

Voltage across 2Ω at 2nd loop,

$$I = \frac{V}{R} = \frac{4}{5}$$

$$\therefore V_2 = IR$$

$$\rightarrow V_2 = \frac{4}{5} \times 2 = \frac{8}{5}$$

∴

$$V_3 = 4$$

So,


$$\begin{aligned} P.d &= V_1 + V_2 + V_3 \\ &= \frac{15}{7} + \frac{8}{5} + 4 \end{aligned}$$

(1) →


$$7.74V$$

Ans

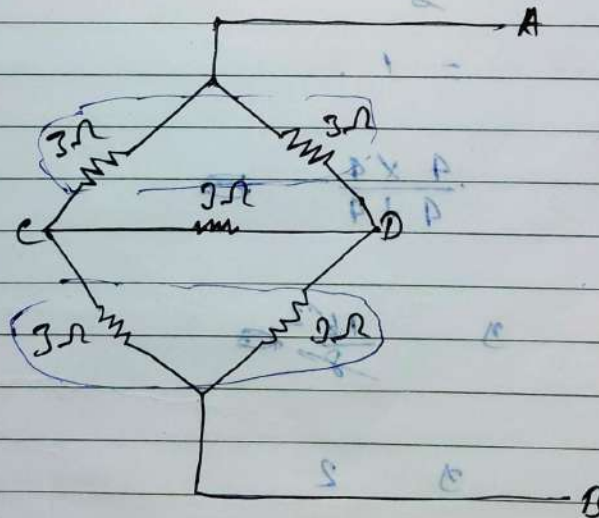
Qn) find the equivalent resistance between terminal A and B?



Soln

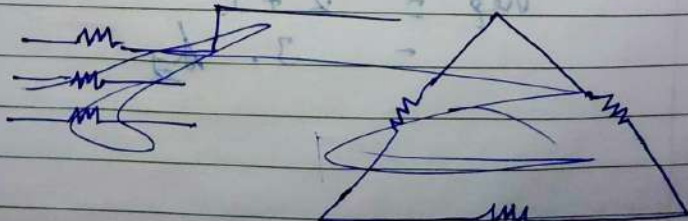

Soln.

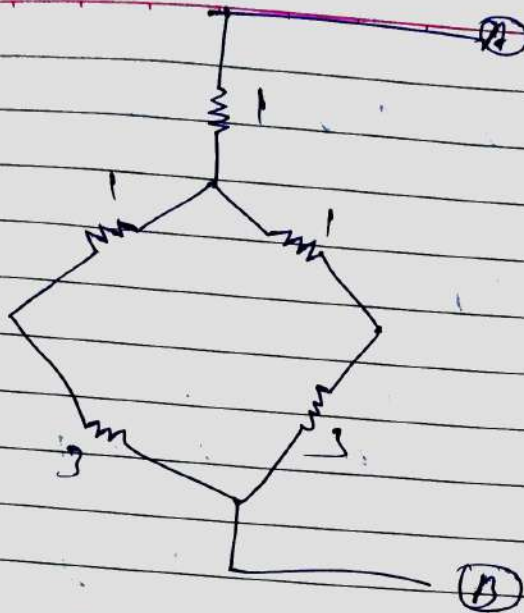

$$Z_0 = \frac{Z_D}{3}$$

$$= \frac{3}{3}$$

$$= 1$$

Now,

$$\frac{4 \times 4}{4 + 4}$$

$$= \frac{16}{8}$$

$$= 2$$

$$R_{eq} = 2 + 1$$

$$= 3 \Omega$$

Unit :- II


AC Circuit

Date |

Page |

- i.) Three phase balance & unbalance system
- ii.) Relation b/w line voltage & phase voltage in star connected system
- iii.) Relation b/w line current & phase current in delta connected
- iv.) Measurement of power by 2 wattmeter method

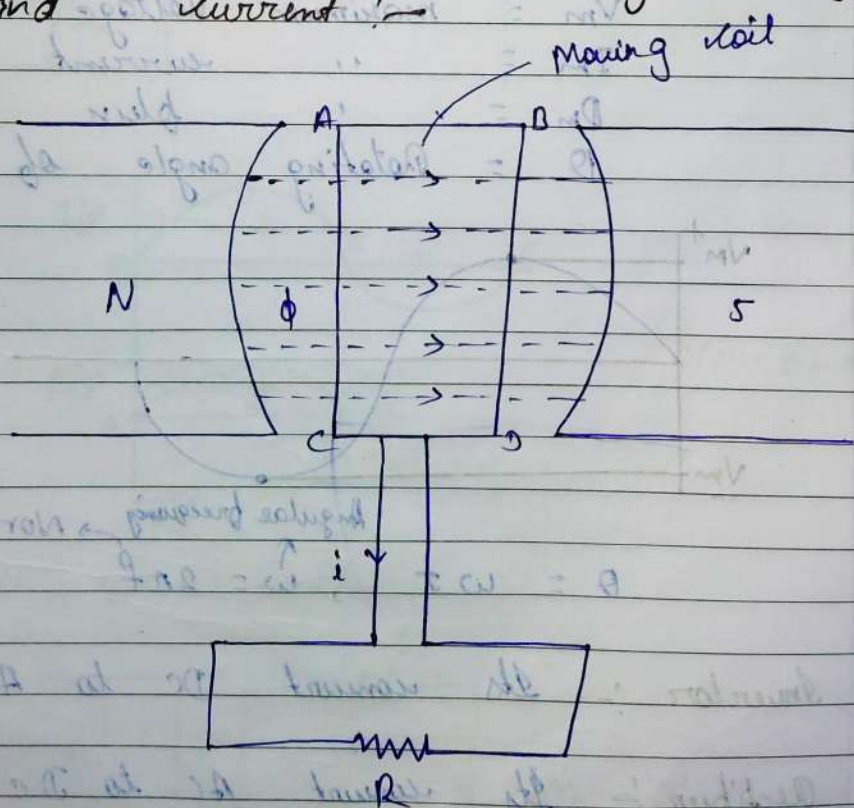★) Generation of alternating voltage and current :-



When a coil ABCD rotating in a uniform magnetic field according to Faraday's law of electromagnetic induction an emf will be induced in that coil.

*.) Generation of alternating voltage and current :-

$$V = V_m \sin \theta$$

$$i = I_m \sin \theta$$

$$\phi = \phi_m \sin \theta$$


where,

V_m = maximum voltage

I_m = " current

ϕ_m = " flux

θ = Rotating angle of coil.

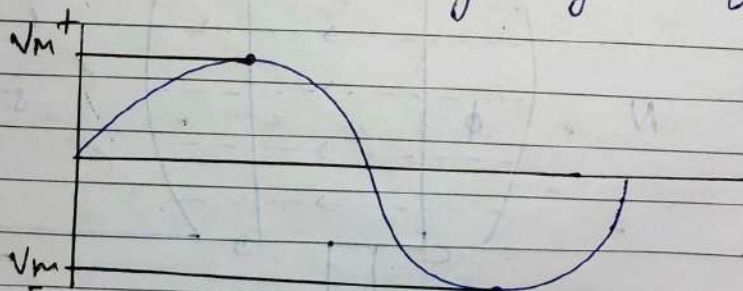

$$\theta = \omega t \quad \begin{matrix} \uparrow \\ \text{Angular frequency} \end{matrix} \quad \begin{matrix} \rightarrow \\ \text{Normal frequency} \end{matrix} \quad \omega = 2\pi f$$



*.) Inverter :- Its convert DC to AC

*.) Rectifier :- Its convert AC to DC

There are basically three types of Rectifier :-


- i.) Half Wave Rectifier
- ii.) Full Wave Rectifier
- iii.) Bridge Rectifier


i.) Half Wave Rectifier :-

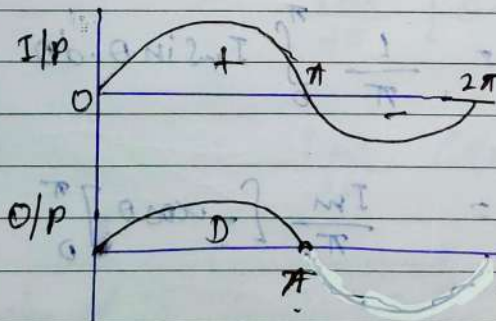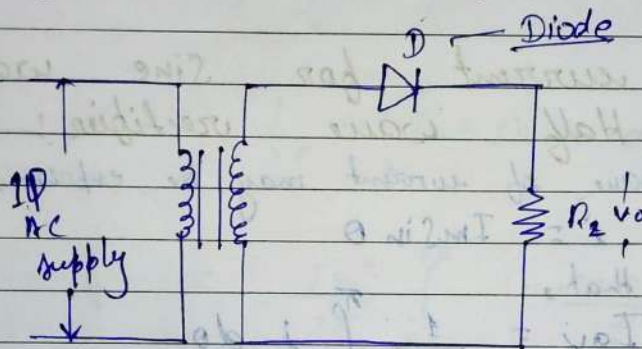

O/P :- 0 - π

ii.) Full Wave Rectifier

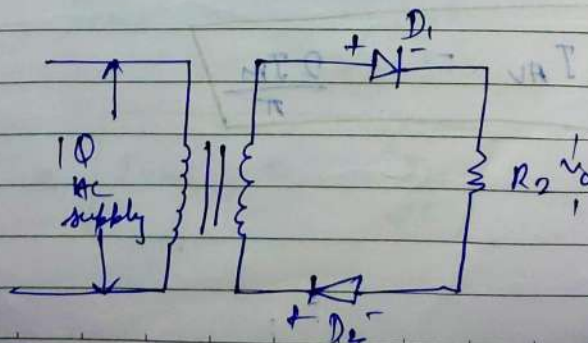

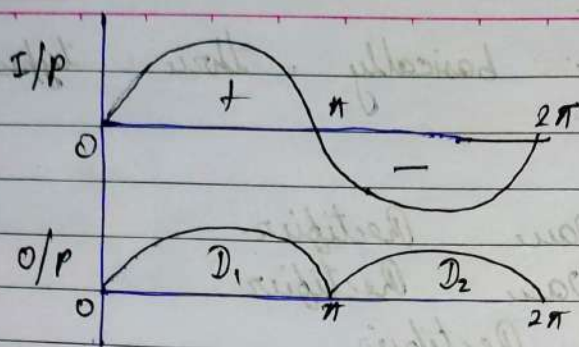

O/P :- $0 - 2\pi$

MST ★

Average current for sine wave
for Half wave rectifier:

A sine wave of current may be expressed as,

$$i = I_m \sin \theta$$

∵ we know that,

$$I_{AV} = \frac{1}{\pi} \int_0^{\pi} i \cdot d\theta$$

$$I_{AV} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta \cdot d\theta$$

$$= \frac{I_m}{\pi} \left[-\cos \theta \right]_0^{\pi}$$

$$= \frac{-I_m}{\pi} (-1 - 1)$$

$$I_{AV} = \frac{2 I_m}{\pi}$$

10
10
10
39

Date |

Page |

★ RMS current for sine wave for full wave rectifier :-

$$I_{rms} = \sqrt{\text{Mean Value of } i^2} \quad \text{--- (1)}$$

Mean value of i^2 ,

$$= \frac{1}{2\pi} \int_0^{2\pi} i^2 \cdot d\theta$$

$$= \frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \theta \cdot d\theta$$

$$= \frac{I_m^2}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\theta}{2} d\theta$$

$$= \frac{I_m^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi}$$

$$= \frac{I_m^2}{4\pi} \left(2\pi - \frac{\sin 4\pi}{2} - 0 - 0 \right)$$

$$\text{Mean value of } i^2 = \frac{I_m^2}{2}$$

from eqn (i)

$$\therefore I_{rms} = \sqrt{\frac{I_m^2}{2}}$$

$$\Rightarrow I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

* Form Factor :-

The form factor of an alternating current wave shape is defined as the ratio of its rms value to the average value.

$$\text{form factor} = \frac{I_{rms}}{I_{av}}$$

$$= \frac{I_m / \sqrt{2}}{\frac{2 I_m}{\pi}}$$

$$= \frac{I_m}{\sqrt{2}} \times \frac{\pi}{2 I_m}$$

$$= \frac{\pi}{2 \sqrt{2}}$$

* Peak factor :- (crest factor) :-

The peak factor of an alternating current wave shape is defined as the ratio of its maximum value to the rms value.

$$\text{Peak factor (C.F.)} = \frac{I_m}{I_{rms}}$$

$$= \frac{I_m}{I_m / \sqrt{2}}$$

$$= 1.414.$$


★.) Reactance :- (X) :-

There are basically two types of reactance :-

i.) Inductive Reactance (X_L)

ii.) Capacitive Reactance (X_C)
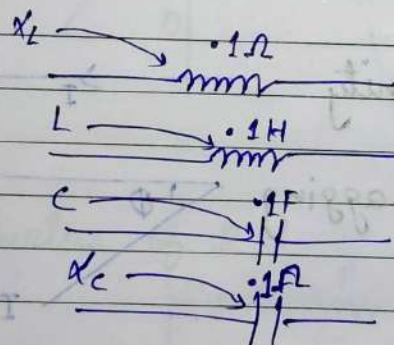
$$X = \begin{cases} X_L = \omega L = 2\pi f L \rightarrow \text{Henry} \\ X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \rightarrow \text{ohm} \end{cases}$$



Units :-


$$\begin{aligned} X_L &= \Omega \\ L &= \text{Henry} \\ X_C &= \Omega \\ C &= \text{farad} \end{aligned}$$

★.) Impedance :-

$$Z = \sqrt{R^2 + X^2}$$

$\downarrow \quad \quad \downarrow \quad \downarrow$
 $\Omega \quad \quad \Omega \quad \Omega$

Impedance triangle :-

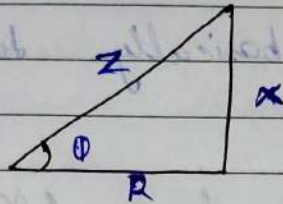


$$Z = \sqrt{R^2 + X^2}$$

Note:-

Power factor ($\cos \phi$) = $\frac{R}{Z}$




Power factor = $\cos \phi = 1$

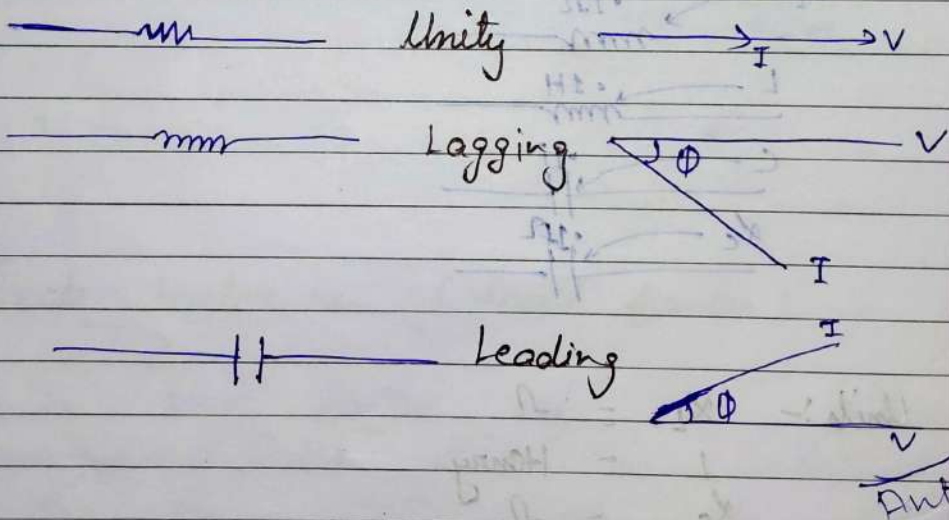


*.) Properties of R, L & C :-

1.) Properties of R :-

AC through pure resistive circuit

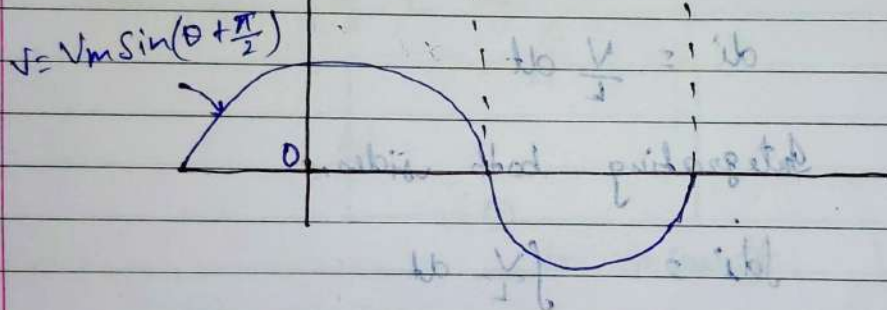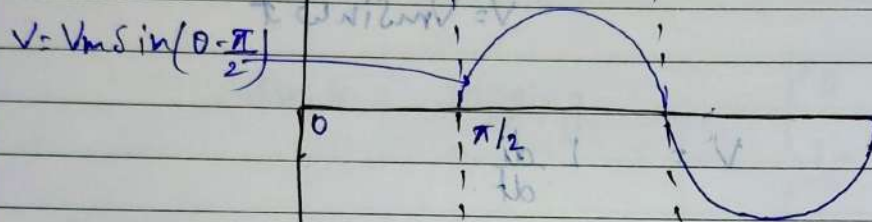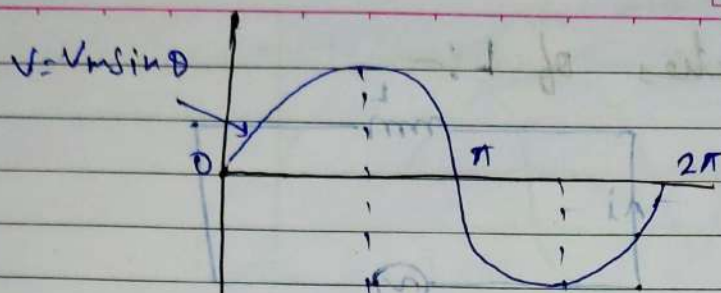


→ Properties of R:-

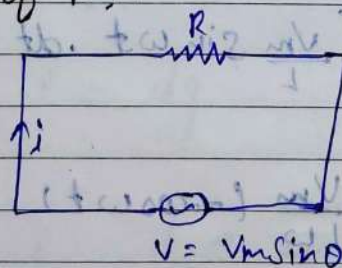

$$V = iR$$

$$i = \frac{V_m \sin \theta}{R}$$

$$i = I_m \sin \theta$$

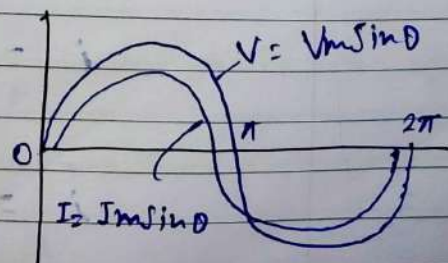


$$I = I_m \sin \theta$$

$\phi = 0$

$\cos \phi = 1 \Rightarrow \text{Unity}$

Properties of L:-

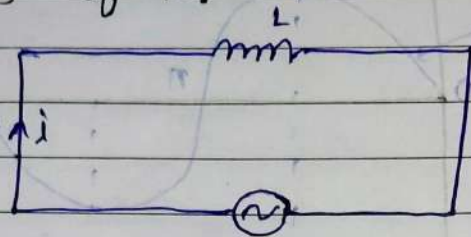

$$V = V_m \sin \omega t$$

$$V = L \frac{di}{dt}$$

$$di = \frac{V}{L} dt$$

Integrating both sides,

$$\int di = \int \frac{V}{L} dt$$


$$i = \int \frac{V_m}{L} \sin \omega t \cdot dt$$

$$i = \frac{V_m}{L\omega} (-\cos \omega t)$$


$$i = \frac{V_m}{L\omega} \sin(\omega t - \pi/2)$$

$$i = \frac{V_m}{X_L} \sin(\omega t - \pi/2) \quad \left[\because X_L = \omega L \right]$$

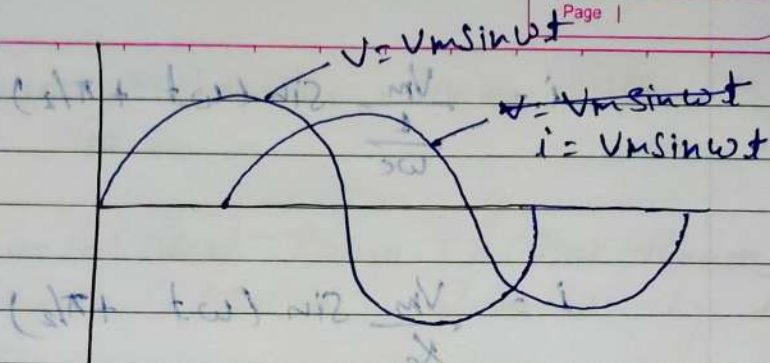
$$i = I_m \sin(\omega t - \pi/2) \quad \left[\because \frac{V_m}{X_L} = I_m \right]$$



$\cos \phi = \text{lagging}$

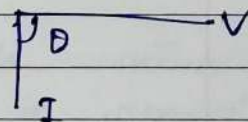

Properties of C :-

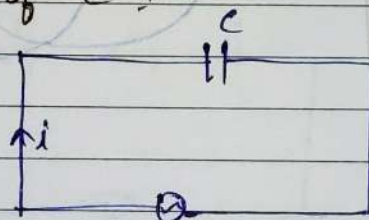

$$V = V_m \sin \omega t$$

$$q = CV$$

$$i = \frac{dq}{dt}$$

$$i = \frac{d}{dt} CV$$


$$i = \frac{d}{dt} C V_m \sin \omega t$$

$$i = C V_m \omega \cos \omega t$$


$$i = C V_m \omega \sin (\omega t + \pi/2)$$

$$i = \frac{V_m}{\frac{1}{\omega C}} \sin(\omega t + \pi/2)$$
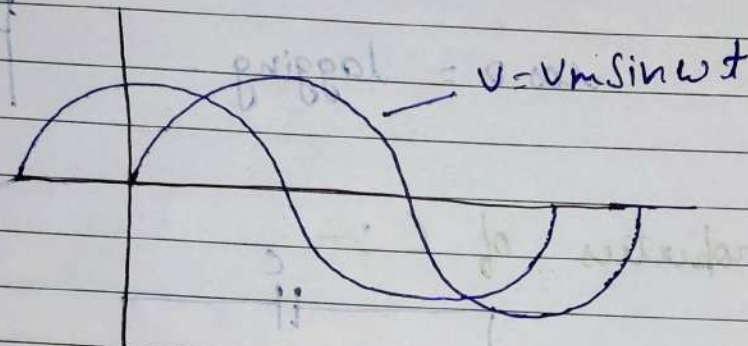
$$i = \frac{V_m}{X_C} \sin(\omega t + \pi/2) \quad \left[\because \frac{1}{\omega C} = X_C \right]$$



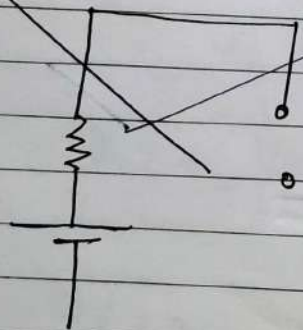Q.1) Find power in 8.2 resistor by Thevenin theorem connected across AB.



$$V_{th} = 8$$

$$R_{th} = 8$$

$$P = \frac{V_{th}^2}{R_{th} + R_L}$$


$$P = \frac{8^2}{8 + 8.2}$$

$$P = 0.47 \text{ W}$$

* Active Power, Reactive Power and Apparent Power :-

Active Power :- (Real Power) / (True Power) / (Output Power) / (Power absorbed by the circuit) :-

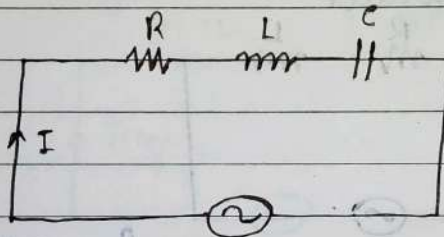
It is the power which is actually consumed in the circuit (or in resistor) and its unit is watt and denoted by 'P'.



$$P = V_{rms} I_{rms} \cos \phi$$

$$P = (V I \cos \phi) \text{ , watt}$$

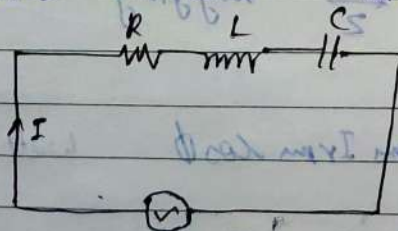Reactive Power :- It is the power taken by the reactance of the circuit. This power is not actually consumed but it flows forth and back between source and load and denoted by 'Q'.



{ Unit is, Volt
Amperes reactive
(VAr) }


$$Q = V_{rms} I_{rms} \sin \phi$$

$$Q = V I \sin \phi \text{ , VAr}$$


11) Apparent Power :- It is given by the product of r.m.s value of voltage and current and denoted by "S" and unit is Volt Ampere (VA).

$$S = V_{rms} I_{rms}$$

$$S = (VI) \text{ VA}$$

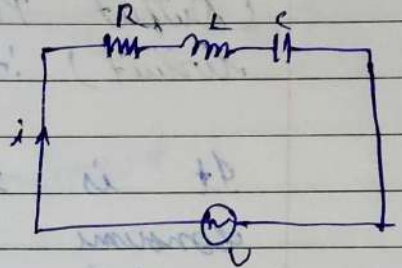

★) Series RL circuit

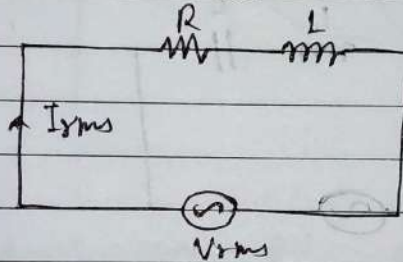

$$f = 50 \text{ Hz}$$

(Inductive Reactance) ① $X_L = 2\pi f L$ Ω

(Impedance) ② $Z = \sqrt{R^2 + X_L^2}$ Ω

(Current) ③ $I_{rms} = \frac{V_{rms}}{Z}$ A

(Power factor) ④ $\cos \phi = \frac{R}{Z}$ lagging

(Active Power) ⑤ $P = V_{rms} I_{rms} \cos \phi$ Watt

(Reactive Power) ⑥ $Q = V_{rms} I_{rms} \sin \phi$ VAR

(Apparent power) ⑦ $S = V_{rms} I_{rms}$ VA


$$(8) \quad V_p = I_{rms} \times R \quad \text{--- cost} \quad (10)$$

$$(9) \quad V_L = I_{rms} \times X_L \quad \text{--- P.S.O}$$

Note :- When $R \& L$ comes in the circuit then the circuit is lagging. (2)

When $R \& C$ comes in the circuit then the circuit is leading. (3)

Ques

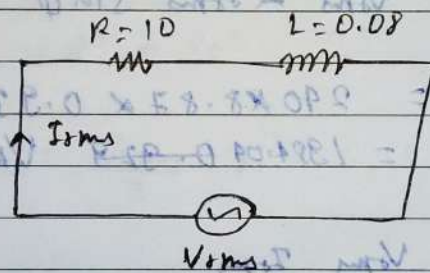

Soln

$$(1) \quad X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 0.08 = 25.13 \, \Omega$$

$$(2) \quad Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + (25.13)^2} = 27.04 \, \Omega$$

$$(3) \quad \cos \phi = \frac{R}{Z} = \frac{10}{27.04} = 0.369 \text{ lagging.}$$

$$(4) \quad I_{rms} = \frac{V_{rms}}{Z} \quad (8)$$

$$= \frac{240}{0.289} = 8.37 \text{ A} \quad (9)$$

$$(5) \quad P = V_{rms} I_{rms} \cos \phi$$

$$= 240 \times 8.37 \times 0.93$$

$$= 185.52 \text{ Watt}$$

$$(6) \quad Q = V_{rms} \times I_{rms} \sin \phi$$

$$= 240 \times 8.37 \times 0.93$$

$$= 1984.04 \text{ VAR}$$

$$(7) \quad S = V_{rms} I_{rms}$$

$$= 240 \times 8.37$$

$$= 2008.8 \text{ VA}$$

$$(8) \quad V_R = I_{rms} \times R$$

$$= 8.37 \times 10$$


$$= 83.7 \text{ Volt}$$

$$(9) \quad V_L = I_{rms} \times X_L$$

$$= 8.37 \times 25.13$$

$$= 210.34 \text{ Volt}$$

#1) Series RC circuit :-

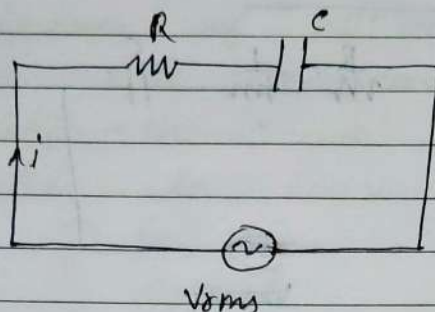

$$(1) X_C = \frac{1}{2\pi f C} \Omega$$

$$(2) Z = \sqrt{R^2 + X_C^2} \Omega$$

$$(3) I_{rms} = \frac{V_{rms}}{Z} A$$

$$(4) \cos \phi = \frac{R}{Z} \text{ leading}$$

$$(5) P = V_{rms} I_{rms} \cos \phi \text{ watt}$$

$$(6) Q = V_{rms} I_{rms} \sin \phi \text{ VAR}$$

$$(7) S = V_{rms} I_{rms} \text{ VA}$$

$$(8) V_R = I_{rms} \times R \text{ volt}$$

$$(9) V_C = I_{rms} \times X_C \text{ volt}$$

$$(3) \quad Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \Omega \quad \text{(Impedance)}$$

$$(4) \quad I_{rms} = \frac{V_{rms}}{Z} \quad A \quad \text{(Current)}$$

$$(5) \quad \cos \phi = \frac{R}{Z} \quad \begin{array}{l} X_L > X_C \text{ — lagging} \\ X_C > X_L \text{ — leading} \end{array} \quad \text{(Power factor)}$$

$$(6) \quad P = V_{rms} I_{rms} \cos \phi \quad \text{Watt} \quad \text{(Active power)}$$

$$(7) \quad Q = V_{rms} I_{rms} \sin \phi \quad \text{VAR} \quad \text{(Reactive power)}$$

$$(8) \quad S = V_{rms} I_{rms} \quad \text{VA} \quad \text{(Apparent power)}$$

$$(9) \quad V_R = I_{rms} \times R \quad \text{volt}$$

$$(10) \quad V_L = I_{rms} \times X_L \quad \text{volt}$$

$$(11) \quad V_C = I_{rms} \times X_C \quad \text{volt}$$

Qn) A choke coil having a resistance of 10Ω and inductance of 0.05 Henry is connected in series with a condenser of $10\mu F$ is connected in a circuit. The whole circuit has been connected to $200V$, $50Hz$ frequency.

- Calculate:
- (i) Impedance
 - (ii) Current
 - (iii) Power factor
 - (iv) Output power (Active power).
 - (v) Apparent power
 - (vi) Reactive power.

Soln

$$R = 10\Omega$$

$$L = 0.05H$$

$$C = 10\mu F = 10 \times 10^{-6}F$$

$$V_{rms} = 200V$$

$$\begin{aligned} X_L &= 2\pi fL \\ &= 2 \times 3.14 \times 0.05 \times 50 \\ &= 15.7\Omega \end{aligned}$$

$$X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{2 \times 3.14 \times 50 \times 10 \times 10^{-6}}$$

$$= \frac{1}{3.14 \times 10^{-5}}\Omega = 31.83\Omega$$

$$(1) \text{ Impedance, } (Z) = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(10)^2 + (15.7 - 31.83 \times 10^{-5})^2}$$

$$= \sqrt{100 + (-246.42) 260 \cdot 17}$$

$$= \frac{251.42}{18.98}$$

$$(2) \text{ Current } (I_{rms}) = \frac{V_{rms}}{Z}$$

$$= \frac{200}{18.98} = 10.53$$

$$(3) \text{ Power factor } (\cos \phi) = \frac{R}{Z} = \frac{10}{18.98}$$

$$= 0.526$$

$$(4) \text{ Active power } (P) = V_{rms} I_{rms} \cos \phi$$

$$= 200 \times 10.53 \times 0.526$$

$$= 1107.756$$

$$(5) \text{ Apparent power } (S) = V_{rms} I_{rms}$$

$$= 200 \times 10.53$$

$$= 2106$$

$$(6) \text{ Reactive power } (Q) = V_{rms} I_{rms} \sin \phi$$

$$= 200 \times 10.53 \times \sin(\cos^{-1} 0.526)$$

$$= 1792.27$$

(Q₁) A coil of inductance 0.08 H negligible resistance is connected in series with a non inductive resistance is 50Ω . The combined circuit is energised is 240 volt . 50 Hz frequency calculate,

- (i) Reactance of the coil.
- (ii) Impedance
- (iii) Current
- (iv) Power factor
- (v) Power factor Active power
- (vi) Reactive power

Solⁿ → Given,

$$L = 0.08 \text{ H}$$

$$R = 50 \Omega + 0 = 50 \Omega$$

$$f = 50 \text{ Hz}$$

$$V_{\text{rms}} = 240 \text{ Volt}$$

$$\begin{aligned} \text{(i)} \quad \therefore X_L &= 2\pi fL \\ &= 2 \times 3.14 \times 50 \times 0.08 \\ &= 25.12 \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad Z &= \sqrt{R^2 + (X_L)^2} \\ &= \sqrt{(50)^2 + (25.12)^2} \\ &= 55.26 \end{aligned}$$

$$\text{(iii)} \quad I_{\text{rms}} = \frac{240}{55.26} \approx 4.34$$

$$(iv) \text{ Power factor } (\cos \phi) = \frac{R}{Z} = \frac{50}{29.26}$$

$$= 1.7088$$

$$(v) \text{ Active power (P)} = V_{rms} I_{rms} \cos \phi$$

$$= 240 \times 8.202 \times 1.7088$$


$$= 3363.73$$

$$(vi) \text{ Reactive power (Q)} = V_{rms} I_{rms} \sin \phi$$

$$= 240 \times 8.202 \times \sin \cos^{-1} 3363.73$$

Ans)

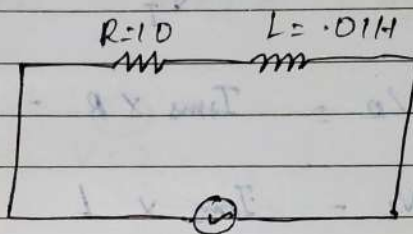A 60 Hz alternating voltage $V = 100 \sin \omega t$ is applied to a series R-L circuit where $R = 10 \Omega$ & $L = 0.01 \text{ H}$. Find the steady state current (I_{rms}) and relative phase angle. Find the voltage drop across each element.



Soln

Given,

$$f = 60 \text{ Hz}$$

$$V = 100 \sin \omega t$$

$$V = 100 \sin \omega t$$

$$V = V_m \sin \omega t$$

$$f = 60 \text{ Hz}$$

$$\therefore V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.7106$$

$$\begin{aligned} \textcircled{1} \quad X_L &= 2\pi fL \\ &= 2 \times \pi \times 60 \times 0.01 \\ &= 3.768 \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{10^2 + (3.768)^2} \\ &= 10.68 \end{aligned}$$


$$\textcircled{3} \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = 6.62$$

$$\textcircled{4} \quad \cos \phi = \frac{R}{Z} = \frac{10}{10.68} = 0.936 \text{ lagging}$$

$$\phi = \cos^{-1} 0.936$$

$$\phi = 20.60^\circ$$

(5)

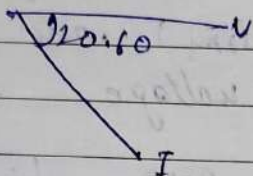

$$(6) V_R = I_{rms} \times R = 66.2 \text{ V}$$


$$(7) V_L = I_{rms} \times L = 24.9 \text{ V}$$

* Complex form and polar form:-

$$10L 5J.13$$

$$6 + 8i$$

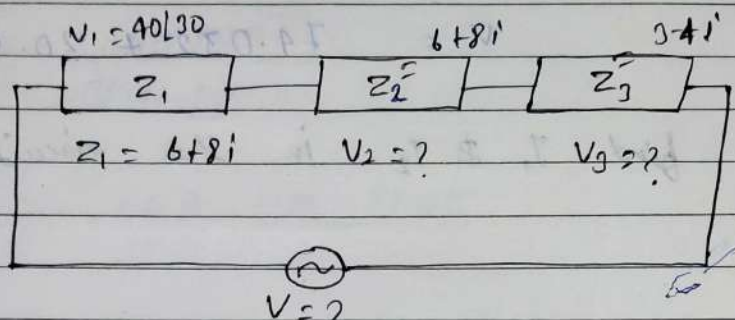Ques find I in this circuit and find V_1 , V_2 & V_3 and also find V



Solu $\Rightarrow$

$$V_1 = I \cdot Z_1$$

$$I = \frac{V_1}{Z_1}$$

$$= \frac{40 \angle 30^\circ}{6 + 8i}$$

$$= \frac{40 \angle 30^\circ}{10 \angle 53.13^\circ}$$

$$= 4 \angle -23.13^\circ$$

$$Z_1 = 6 \angle 0^\circ$$

$$Z_2 = 8 \angle 90^\circ$$

$$Z_1 \times Z_2 = 6 \angle 0^\circ \times 8 \angle 90^\circ$$

$$= 48 \angle 90^\circ$$

$$\frac{Z_1}{Z_2} = \frac{6 \angle 0^\circ}{8 \angle 90^\circ}$$

$$= \frac{3}{4} \angle -90^\circ$$

$$V_2 = I \cdot Z_2$$

$$= 4 \angle -23.13^\circ \times 8 \angle 90^\circ$$

$$= 32 \angle 66.87^\circ$$

$$= 32 \angle 66.87^\circ$$

$$V_2 = 32 \angle 66.87^\circ$$

$\neq$

$$V_3 = I \cdot Z_3$$

$$= 4 \angle -23.13^\circ \times 3 - 4i$$

$$= 4 \angle -23.13^\circ \times 5 \angle -53.13^\circ$$

$$= 20 \angle -76.26^\circ$$

$\times$ - polar
 $+$ - complex

Date |


Page |

$$V = V_1 + V_2 + V_3$$

$$V = 40 \angle 30 + 40 \angle 30 + 20 \angle -76.26 \text{ } \underline{\text{by}}$$

$$V = 74.032 + 20.572 j \text{ } \underline{\text{by}}$$

Ques) find I_1 & I_2 in this circuit

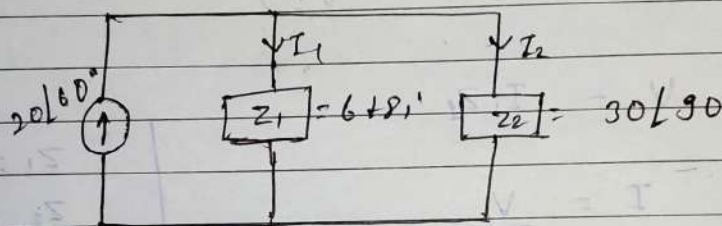

Sol: Using current division Rule,

$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$= \frac{20 \angle 60 \times 30 \angle 90}{(6 + 8j) + 30 \angle 90}$$

$$= \frac{600 \angle 150}{10 \angle 53.12 + 30 \angle 90}$$

$$= \frac{600 \angle 150}{6 + 37.99 j}$$

$$\Rightarrow \frac{600 \angle 150}{6} = 37.99$$

$$\Rightarrow \frac{600}{6} \frac{1150}{+ 37.991}$$

$$\Rightarrow \frac{600}{38.46} \frac{1150}{181.02}$$

$$= \frac{600}{38.46} \frac{1150 - 81.02}{}$$

$$\Rightarrow \frac{600}{38.46} \frac{1068.98}{}$$

$$\Rightarrow 15.60 \frac{1068.98}{}$$

2

$$I_2 = \frac{I \times R_1}{R_1 + R_2}$$

$$= \frac{20160 \times 6 + 81}{6 + 81 + 30290}$$


$$= \frac{20160 \times 1053.13}{1053.13 + 30290}$$

$$\Rightarrow \frac{200}{6.00 + 37.991} \frac{113.13}{}$$

$$\Rightarrow \frac{200}{6 + 37.991} \frac{113.13}{181.02}$$

$$\Rightarrow \frac{200}{38.46} \frac{113.13 - 81.02}{} \Rightarrow 5.20 \frac{32.11}{}$$

*.) Parallel RLC circuit :-

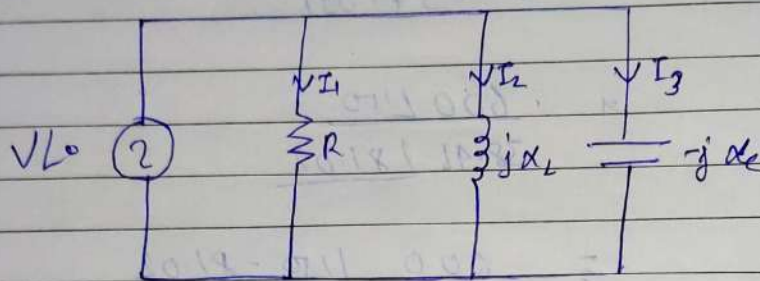


$$I_1 = \frac{V_{L0}}{R}$$

$$I_2 = \frac{V_{L0}}{jX_L}$$

$$= \frac{V_{L0}}{X_L \angle 90^\circ}$$

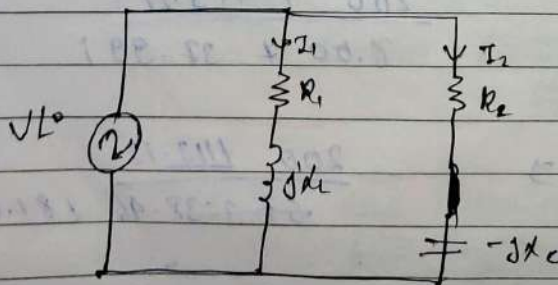
$$I_3 = \frac{V_{L0}}{-jX_C} = \frac{V_{L0}}{X_C \angle -90^\circ}$$



$$I_1 = \frac{VL_0}{R_1 + jX_L}$$

$$I_2 = \frac{VL_0}{R_2 - jX_C}$$

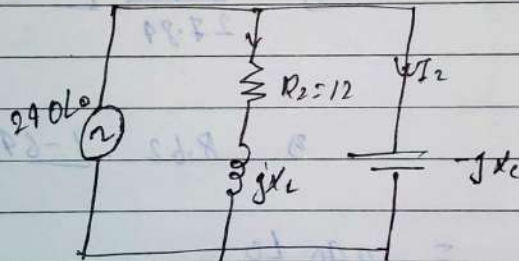Qn. 2) A choke coil of inductor 0.08 H and resistance 12Ω is connected in parallel with a capacitor of $120 \mu\text{F}$ (120×10^{-6}) and combination is connected to supply of 50 Hz frequency. Calculate total current from supply and its power factor.



Soln.

$$X_L = 2\pi fL$$

$$= 2 \times \pi \times 50 \times 0.08$$

$$= 25.12$$

$$X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{2\pi \times 50 \times 120 \times 10^{-6}}$$

$$= 261.7 \quad 26.52$$

Now, $I_1 = \frac{240 \angle 0}{12 + jX_L}$

$$= \frac{240 \angle 0}{\cancel{12} + 25.13 \angle 90}$$

$$\Rightarrow \frac{240 \angle 0}{12 + 25.13j}$$

$$\Rightarrow \frac{240 \angle 0}{27.84 \angle 64.4}$$

$$\Rightarrow \frac{240}{27.84} \angle -64.4$$

$$\Rightarrow 8.62 \angle -64.4$$

2

$$I_2 = \frac{240 \angle 0}{-jX_C}$$

$$= \frac{240 \angle 0}{X_C \angle -90}$$

$$\Rightarrow \frac{240 \angle 0}{26.52 \angle -90}$$

$$\Rightarrow \frac{240}{26.52} \angle 90$$



$$\Rightarrow 9.04 \angle 90$$

$$\Rightarrow I = I_1 + I_2$$




$$= 8.62 \angle -64.4^\circ + 9.04 \angle 90^\circ$$

$$= 3.72 + 1.2j$$

Power factor =

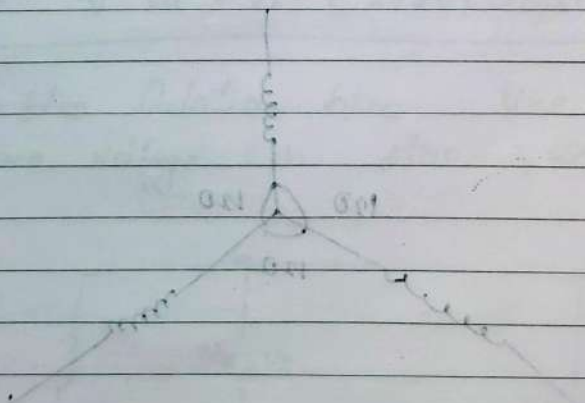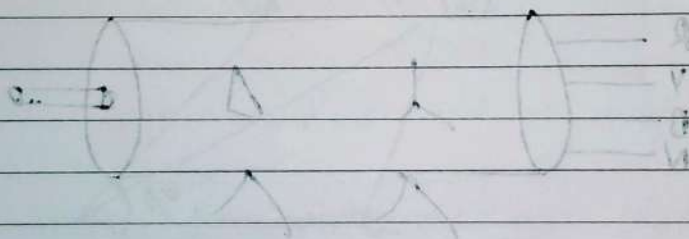


*.) Three phase system :-

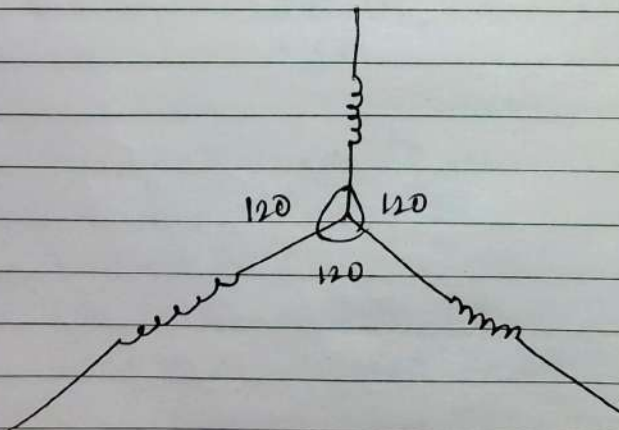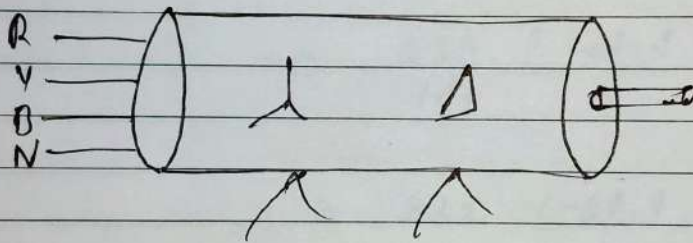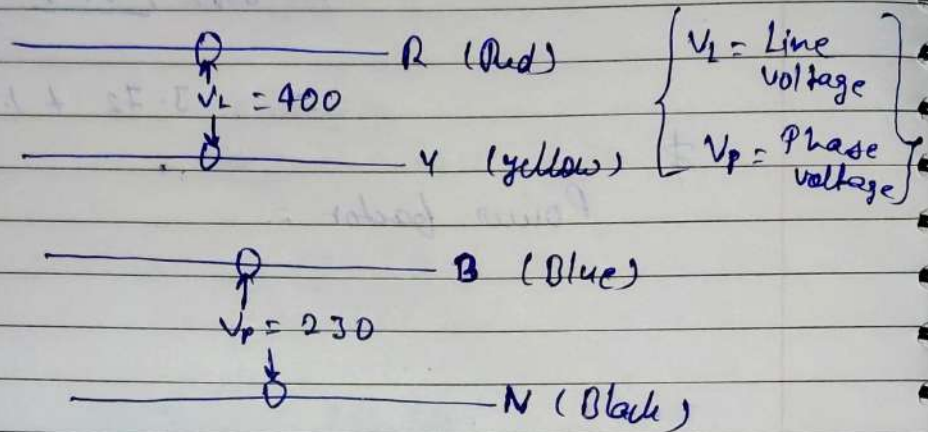


$$\frac{360}{n} = \frac{360}{3} = 120^\circ$$

where,
 $n = \text{No. of phases.}$

★) Phase sequence :-

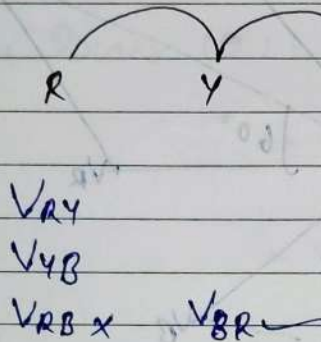

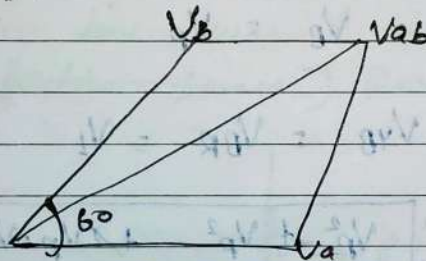★) Law of Parallelogram formula or Resultant formula :-



$$V_{ab} = \sqrt{V_a^2 + V_b^2 + 2V_aV_b\cos 60^\circ}$$

★) Relation b/w line voltage and Phase voltage in star connected system :-

